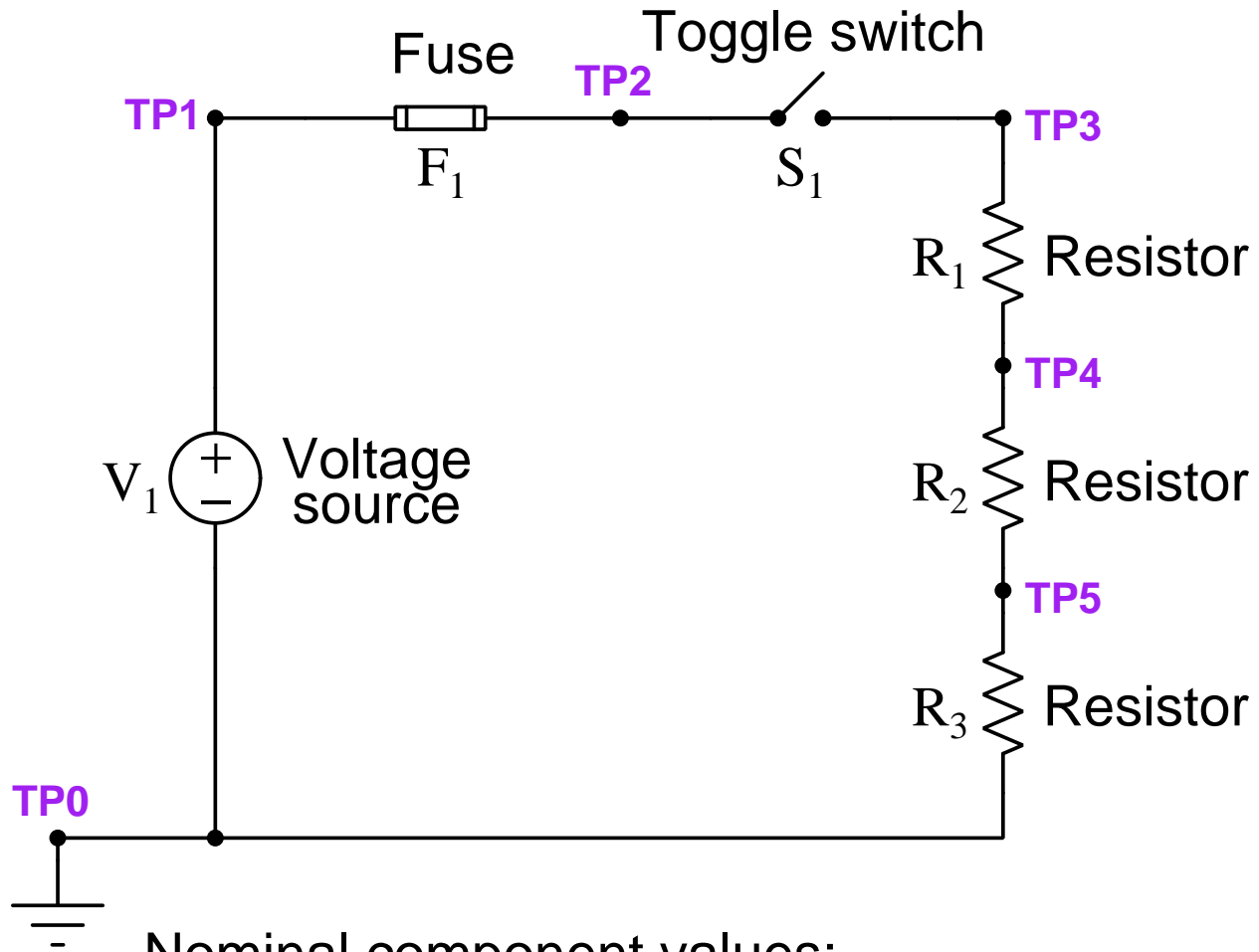


# Circuit #001



Nominal component values:

$$V_1 = \text{_____ Volts +/- _____ \%}$$

$$R_1 = \text{_____ Ohms +/- _____ \%}$$

$$R_2 = \text{_____ Ohms +/- _____ \%}$$

$$R_3 = \text{_____ Ohms +/- _____ \%}$$