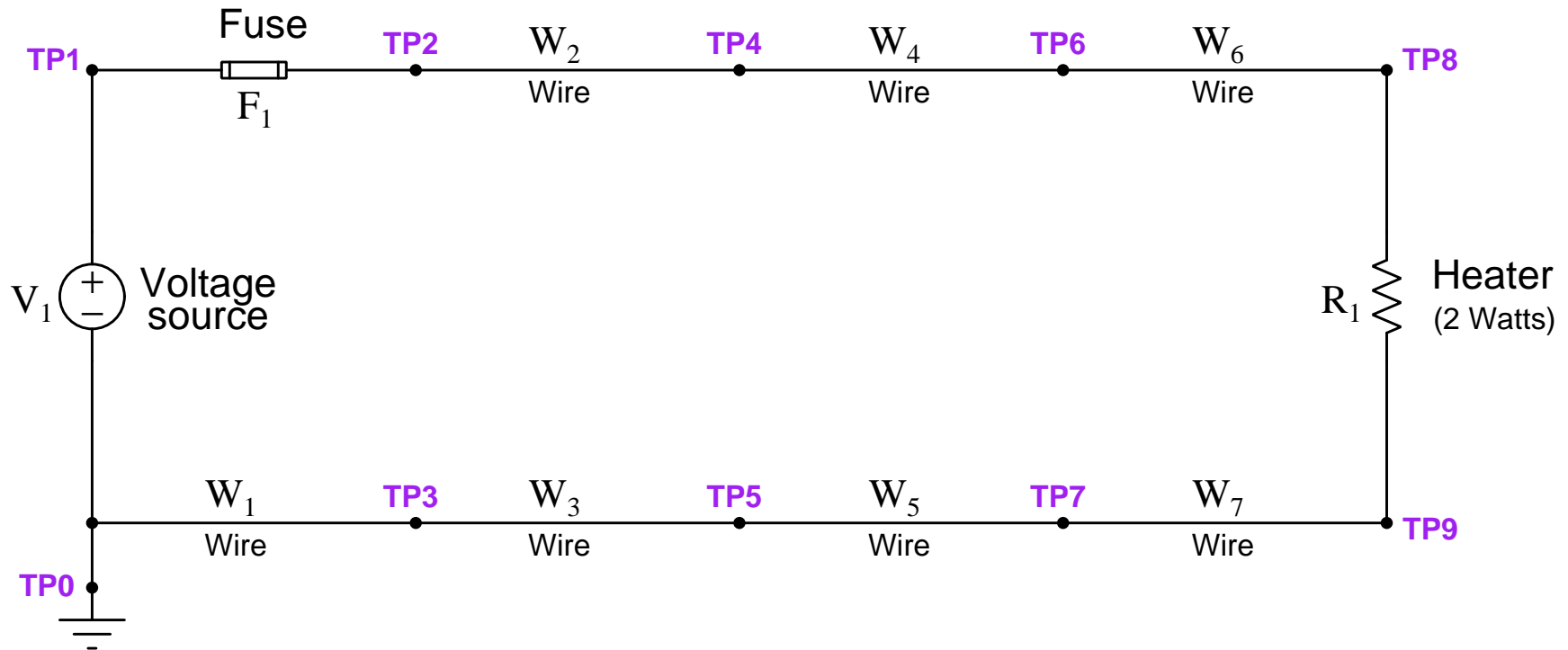


Circuit #000



Nominal component values:

$V_1 =$ _____ Volts +/- _____ %

$R_1 =$ _____ Ohms +/- _____ %