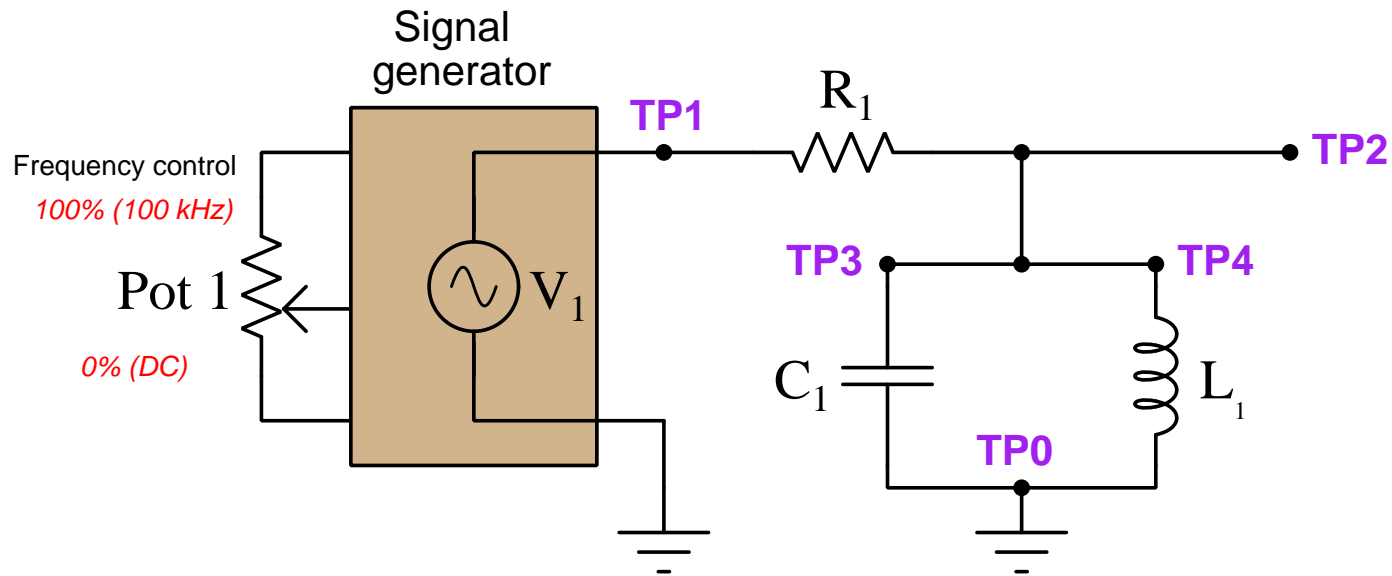


Circuit #010



Nominal component values:

$V_1 =$ _____ Volts +/- _____ %

$R_1 =$ _____ Ohms +/- _____ %

$C_1 =$ _____ μF +/- _____ %

$L_1 =$ _____ mH +/- _____ %