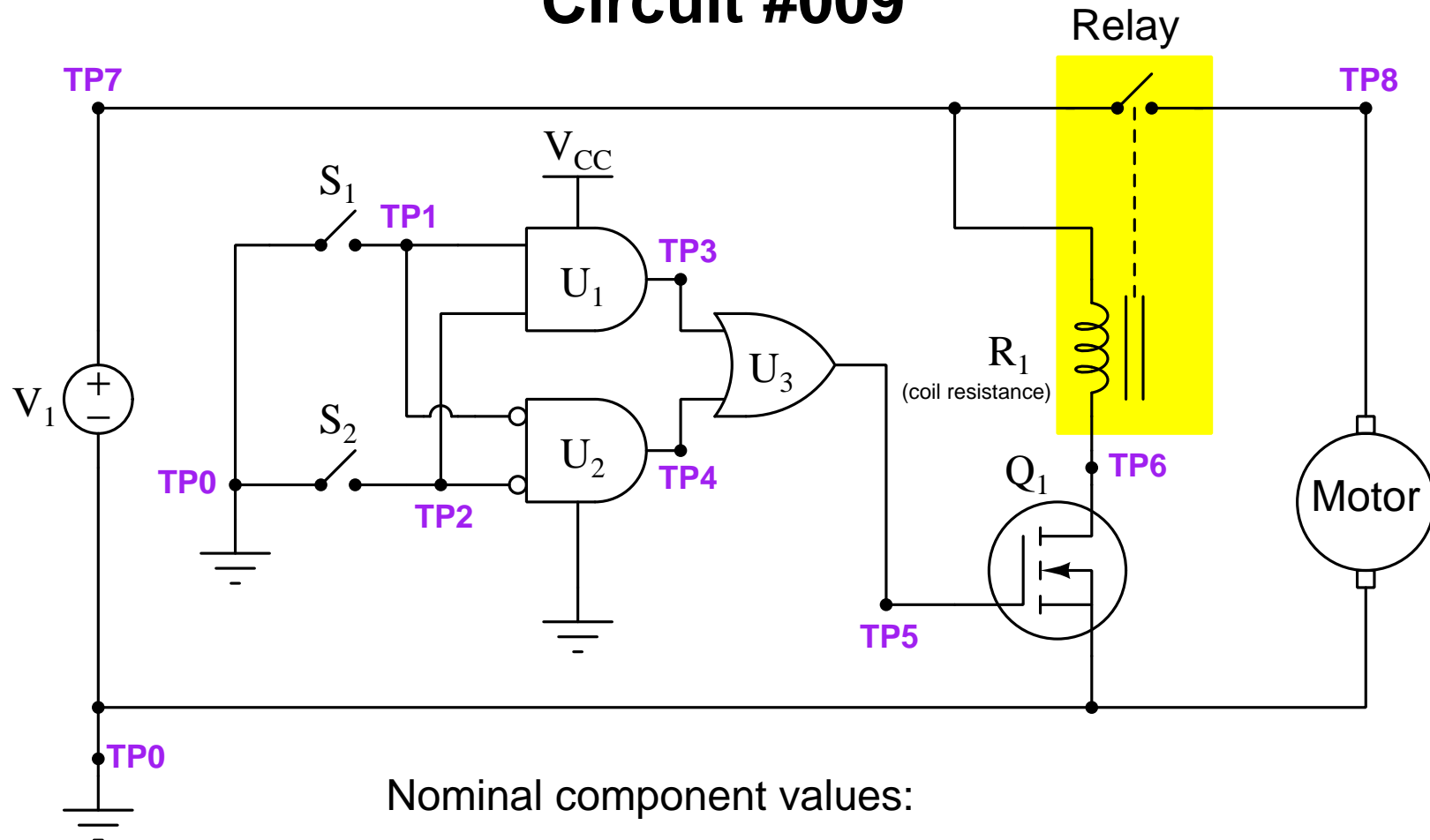


# Circuit #009



Nominal component values:

$$V_1 = \text{_____ Volts +/- _____ \%}$$

$$V_2 (V_{CC}) = \text{_____ Volts +/- _____ \%}$$

$$R_1 = \text{_____ Ohms +/- _____ \%}$$