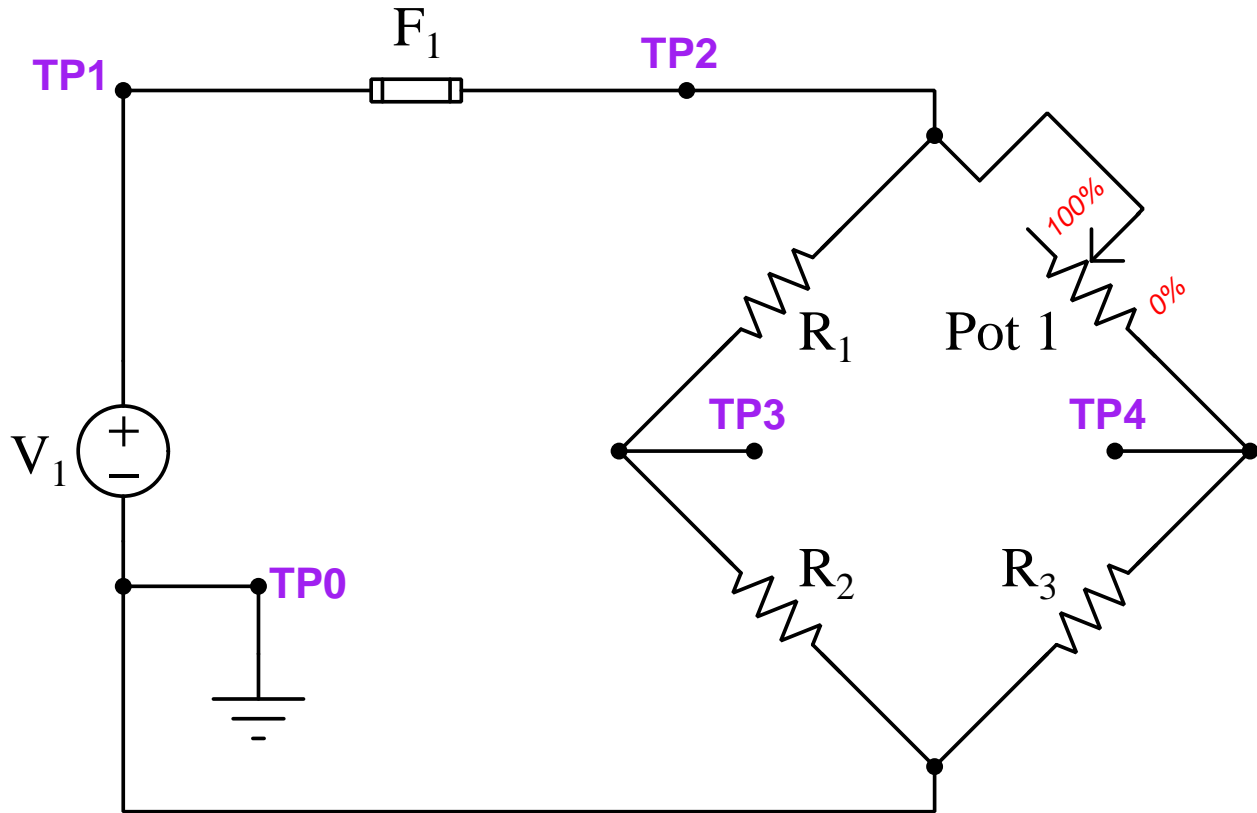


Circuit #005



Nominal component values:

$V_1 =$ _____ Volts +/- _____ %

$R_1 =$ _____ Ohms +/- _____ %

$R_2 =$ _____ Ohms +/- _____ %

$R_3 =$ _____ Ohms +/- _____ %

$R_{\text{pot1}} =$ _____ Ohms +/- _____ %