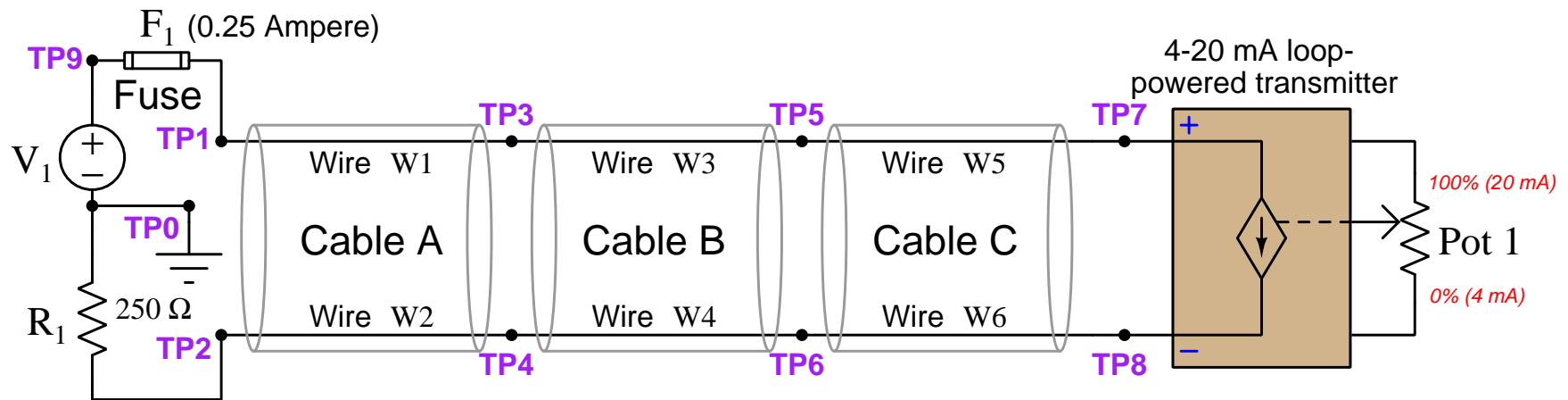


Circuit #006



Nominal component values:

$$V_1 = \text{_____ Volts +/- _____ \%}$$

$$R_{\text{pot1}} = \text{_____ Ohms +/- _____ \%}$$