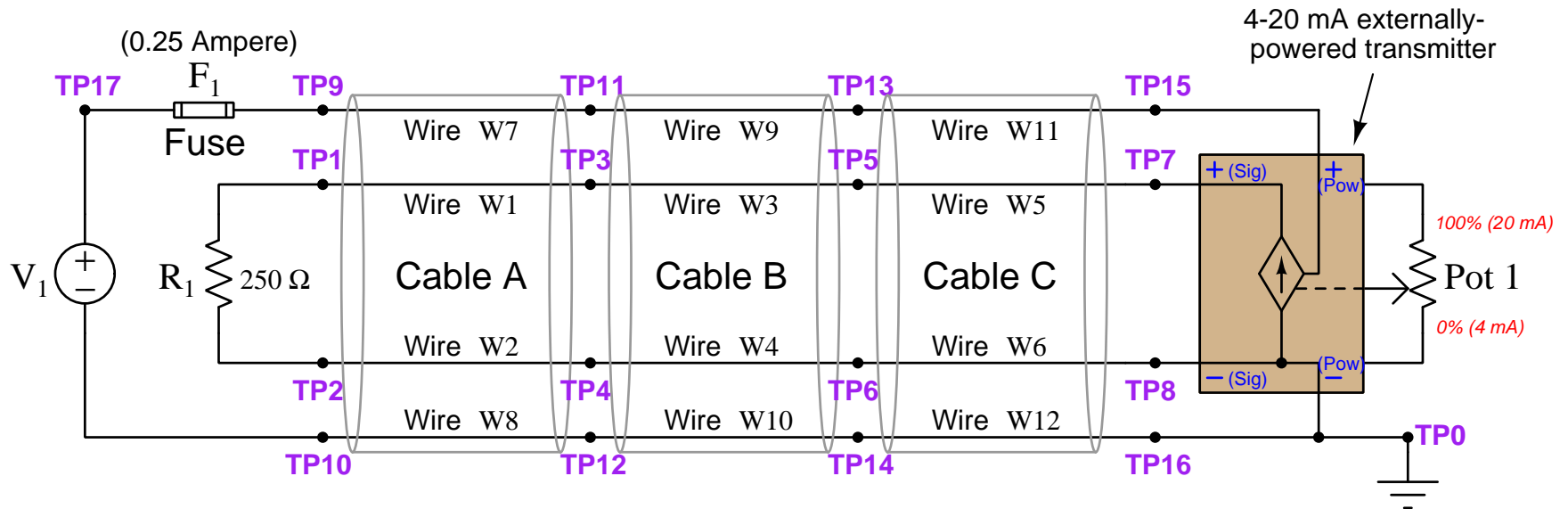


Circuit #007



Nominal component values:

$$V_1 = \text{_____ Volts } +/- \text{ _____ } \%$$

$$R_{\text{pot1}} = \text{_____ Ohms } +/- \text{ _____ } \%$$