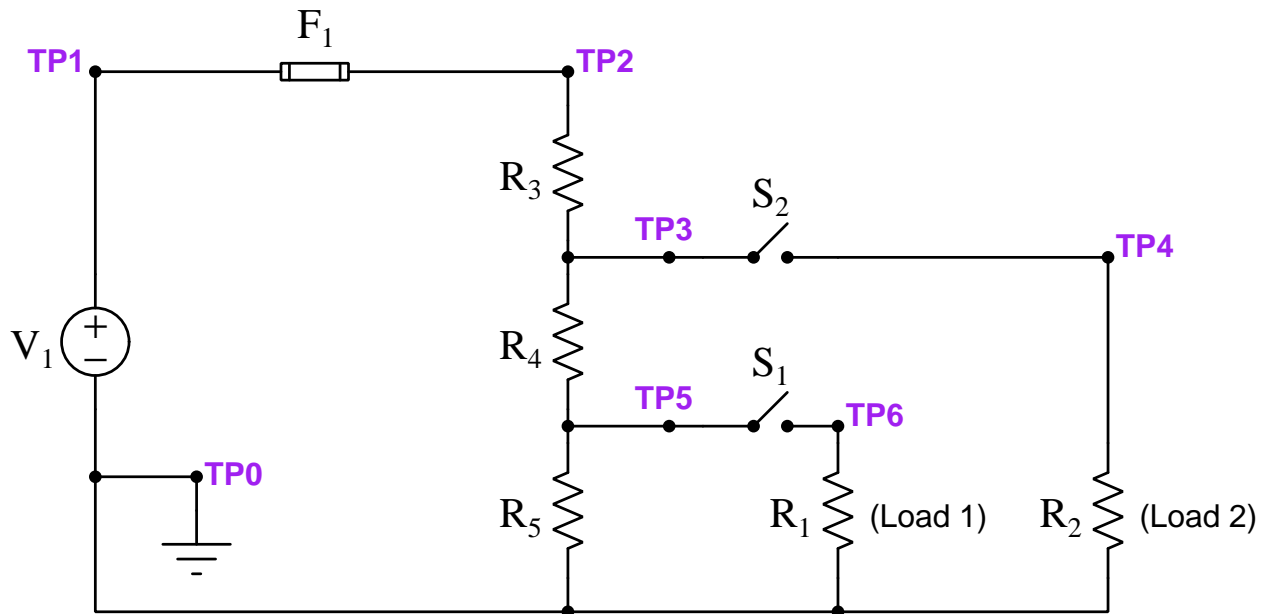


## Circuit #004



Nominal component values:

$V_1 =$  \_\_\_\_\_ Volts +/- \_\_\_\_\_ %

$R_1 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %

$R_2 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %

$R_3 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %

$R_4 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %

$R_5 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %