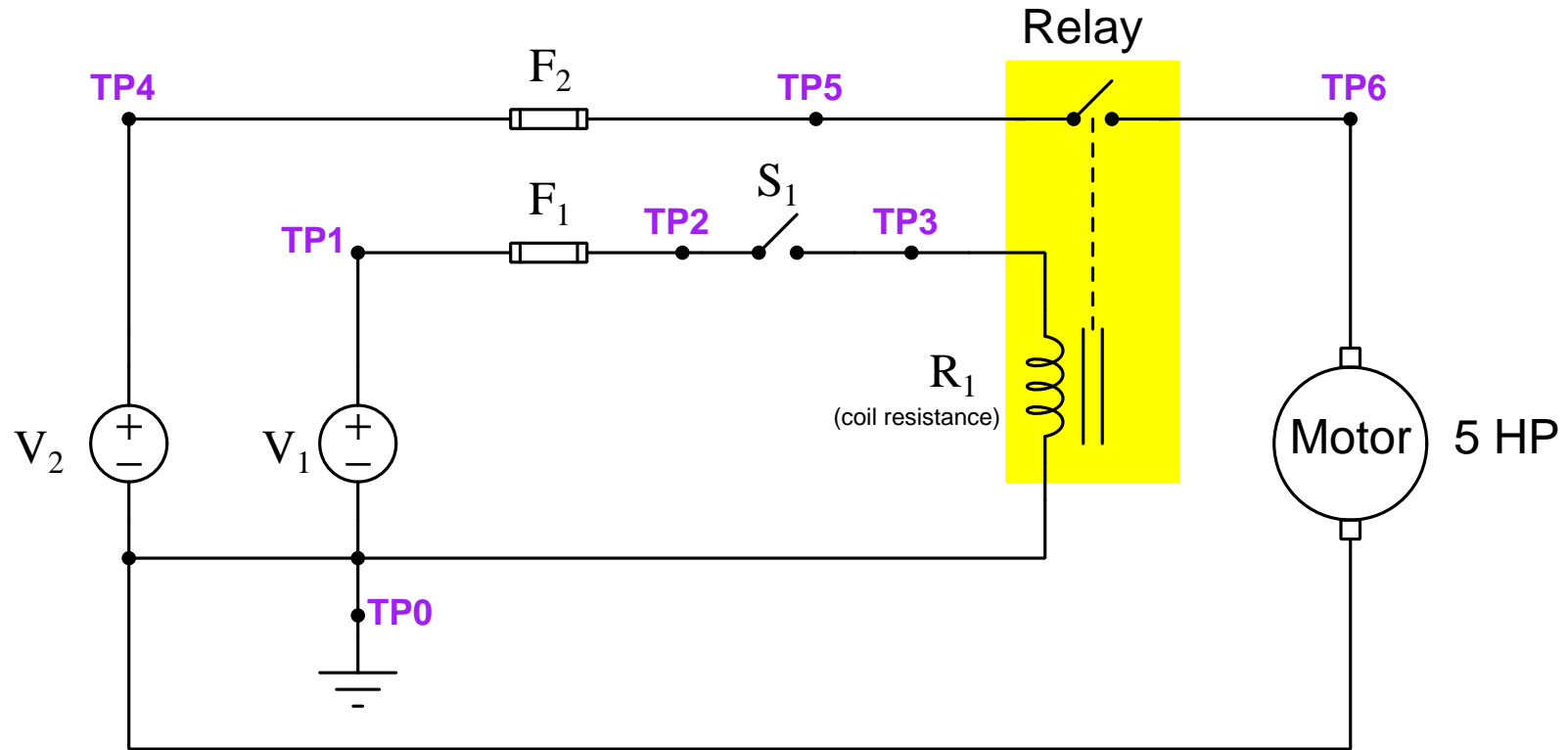


## Circuit #008



Nominal component values:

$V_1 =$  \_\_\_\_\_ Volts +/- \_\_\_\_\_ %

$V_2 =$  \_\_\_\_\_ Volts +/- \_\_\_\_\_ %

$R_1 =$  \_\_\_\_\_ Ohms +/- \_\_\_\_\_ %