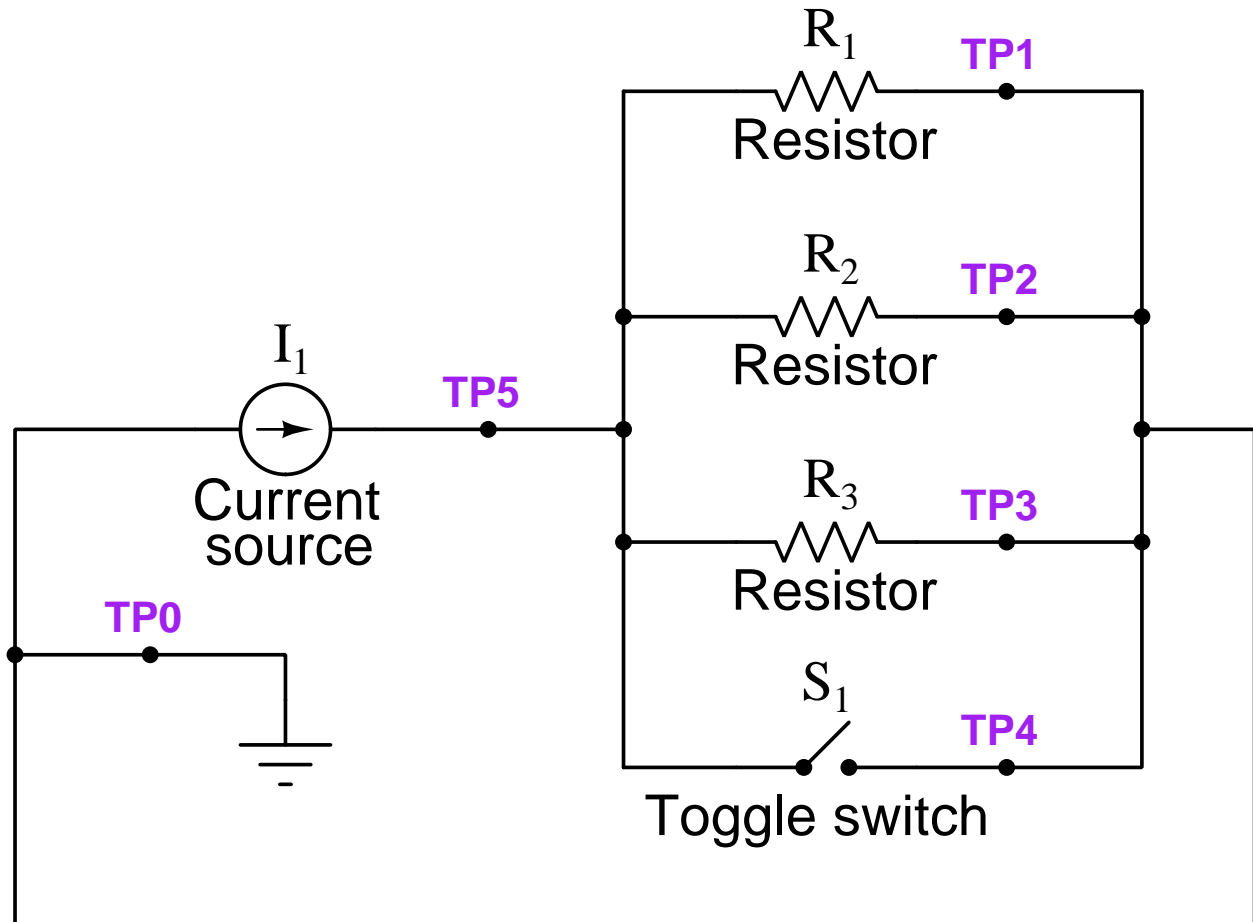


Circuit #002



Nominal component values:

$$I_1 = \text{_____ mA } +/- \text{ _____ \%}$$

$$R_1 = \text{_____ Ohms } +/- \text{ _____ \%}$$

$$R_2 = \text{_____ Ohms } +/- \text{ _____ \%}$$

$$R_3 = \text{_____ Ohms } +/- \text{ _____ \%}$$