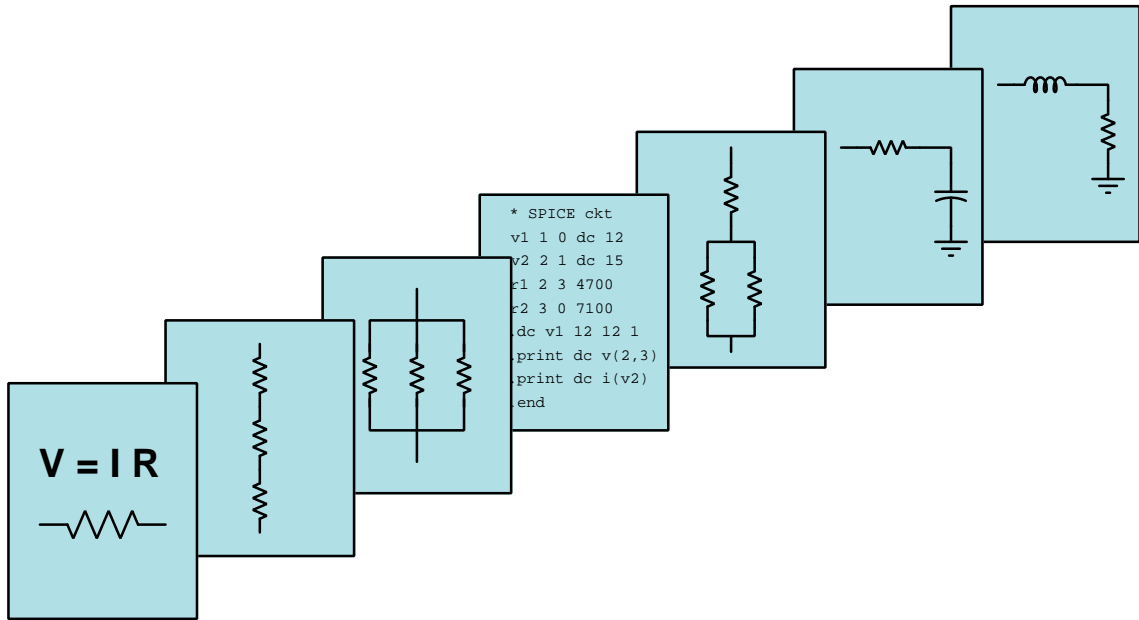


MODULAR ELECTRONICS LEARNING (MODEL) PROJECT



EFFICIENCY AND POWER FACTOR

© 2018-2024 BY TONY R. KUPHALDT – UNDER THE TERMS AND CONDITIONS OF THE
CREATIVE COMMONS ATTRIBUTION 4.0 INTERNATIONAL PUBLIC LICENSE

LAST UPDATE = 10 SEPTEMBER 2024

This is a copyrighted work, but licensed under the Creative Commons Attribution 4.0 International Public License. A copy of this license is found in the last Appendix of this document. Alternatively, you may visit <http://creativecommons.org/licenses/by/4.0/> or send a letter to Creative Commons: 171 Second Street, Suite 300, San Francisco, California, 94105, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

Contents

1	Introduction	3
1.1	Recommendations for students	3
1.2	Challenging concepts related to power factor and efficiency	5
1.3	Recommendations for instructors	6
2	Case Tutorial	7
2.1	Example: bicycle-driven grain mill	8
2.2	Example: bicycle-driven loads	9
2.3	Example: electric versus gasoline car efficiency	10
2.4	Example: RLC circuit power factor	13
2.5	Example: power factor from V,I,P measurements	15
2.6	Examples: power factor correction	16
2.6.1	Given PF, V, I, f	16
2.6.2	Given P, V, I, f	16
2.6.3	Given oscillograph, V, I, f	17
3	Simplified Tutorial	19
4	Full Tutorial	27
4.1	Energy efficiency	27
4.2	Power factor	30
4.3	How power factor affects efficiency	34
4.4	Power factor correction	35
5	Questions	39
5.1	Conceptual reasoning	43
5.1.1	Reading outline and reflections	44
5.1.2	Foundational concepts	45
5.1.3	Unequal heating	47
5.1.4	Misconceptions about AC power	48
5.1.5	Beer analogy for power factor	50
5.2	Quantitative reasoning	51
5.2.1	Miscellaneous physical constants	52
5.2.2	Introduction to spreadsheets	53

CONTENTS	1
5.2.3 Three AC loads	56
5.2.4 Power factor from wattmeter	57
5.2.5 AC generator horsepower	58
5.2.6 Power factor from Lissajous figure	59
5.2.7 Power factor measurement using instrument transformers	61
5.2.8 Hydroelectric generator ratings	62
5.2.9 Power factor for a capacitive circuit	62
5.2.10 Worsening power factor in a motor	63
5.2.11 L versus LC circuit powers	64
5.2.12 Correcting an arbitrary load's power factor	65
5.2.13 Correcting a lagging power factor	66
5.2.14 Correcting a motor's power factor	66
5.2.15 Capacitor array	67
5.3 Diagnostic reasoning	68
5.3.1 Misconceived power factor correction	68
A Problem-Solving Strategies	69
B Instructional philosophy	71
C Tools used	77
D Creative Commons License	81
E References	89
F Version history	91
Index	92

Chapter 1

Introduction

1.1 Recommendations for students

The way in which energy is exchanged between components in an electric power system, especially alternating current (AC) electric power circuits, can be quite confusing. Two related but distinct topics – *efficiency* and *power factor* – are treated together in this module. Although these two concepts are quite distinct from each other, they are often incorrectly conflated, sometimes even treated as one and the same. By exploring these two concepts in the same module, and by demonstrating that they represent two entirely different concepts regarding energy exchange in AC circuits, the hope is that this confusion may averted.

Important concepts related to efficiency and power factor include the **Conservation of Energy**, the **First and Second Laws of Thermodynamics**, **resistance**, **reactance**, **impedance**, **capacitance**, **inductance**, **right-triangle** trigonometry, **phase shift**, **apparent power**, **true power**, **reactive power**, **sine** and **cosine** functions, and **phasor diagrams**.

Here are some good questions to ask of yourself while studying this subject:

- How might an experiment be designed and conducted to explore the concept of power factor in an AC circuit? What hypothesis (i.e. prediction) might you pose for that experiment, and what result(s) would either support or disprove that hypothesis?
- How might an experiment be designed and conducted to explore the concept of power factor correction in an AC circuit? What hypothesis (i.e. prediction) might you pose for that experiment, and what result(s) would either support or disprove that hypothesis?
- What does it mean to say that energy is *conserved*?
- What does it mean when we say that a component *dissipates* energy?
- How does reactance differ from resistance?
- How does impedance relate to resistance and reactance?
- Of what consequence is reactive power in an AC power system?

- Where does the “wasted” energy go in a system that is less than perfectly efficient?
- What is detrimental about an AC circuit with a low efficiency?
- What is detrimental about an AC circuit with a low power factor?
- What differentiates power factor from efficiency?
- Which type of power (reactive, true, or apparent) may be calculated as the simple product of voltage and current?
- What does it mean to say that an AC circuit has a “leading” or a “lagging” power factor?
- What role does an oscilloscope play in the empirical determination of a circuit’s power factor?
- If power factor could somehow be made exactly 100% (1), would poor efficiency matter?
- If efficiency could somehow be made exactly 100% (1), would poor power factor matter?
- How may we redesign a circuit to improve its power factor?
- How may we redesign a circuit to improve its efficiency?

1.2 Challenging concepts related to power factor and efficiency

The following list cites concepts related to this module's topic that are easily misunderstood, along with suggestions for properly understanding them:

- **Resistance versus Reactance versus Impedance** – these three terms represent different forms of opposition to electric current. Despite the fact that they are measured in the same unit (ohms: Ω), they are not the same concept. Resistance is best thought of as electrical *friction*, whereas reactance is best thought of as electrical *inertia*. Whereas resistance creates a voltage drop by dissipating energy, reactance creates a voltage drop by *storing* and *releasing* energy. Impedance is a term encompassing both resistance and reactance, usually a combination of both. Resistance, reactance, and impedance relate to power in the forms of true power (P), reactive power (Q), and apparent power (S).
- **Confusing power factor and efficiency** – these two concepts are definitely related, but not synonymous. Efficiency is a ratio of energy directed out of a system toward useful work versus total energy put in to that system. Power factor, on the other hand, is a ratio of real power (P) to apparent power (S) in an AC circuit.
- **Prime movers** – for any electromechanical generator, the “prime mover” is the mechanical energy source spinning the shaft. Some students mistakenly think the “prime mover” is something *electrical* when it is not. For example, the prime mover for a generator at a hydroelectric power plant is the turbine which is spun by the kinetic energy of falling water.
- **Interpreting oscillograph phase shift** – phase shift is typically expressed in degrees, calculated from the shift between two waves' similar peaks as well as their period. Phase shift may be computed from a time-domain oscillograph, as well as from a Lissajous figure.

The *Case Tutorial* chapter contains examples showing various calculations related to efficiency and to power factor.

1.3 Recommendations for instructors

This section lists realistic student learning outcomes supported by the content of the module as well as suggested means of assessing (measuring) student learning. The outcomes state what learners should be able to do, and the assessments are specific challenges to prove students have learned.

- **Outcome** – Demonstrate effective technical reading and writing

Assessment – Students present their outlines of this module’s instructional chapters (e.g. Case Tutorial, Tutorial, Historical References, etc.) ideally as an entry to a larger Journal document chronicling their learning. These outlines should exhibit good-faith effort at summarizing major concepts explained in the text.

- **Outcome** – Apply the concept of power factor to realistic circuits

Assessment – Calculate the various powers (P , Q , S) and/or power factor for an AC circuit given component values; e.g. pose problems in the form of the “Three AC loads” and “AC generator horsepower” and “Power factor for a capacitive circuit” Quantitative Reasoning questions.

Assessment – Calculate the various powers (P , Q , S) and/or power factor for an AC circuit given empirical measurements; e.g. pose problems in the form of the “Power factor from wattmeter” and “Power factor from Lissajous figure” and “Power factor measurement using instrument transformers” Quantitative Reasoning questions.

- **Outcome** – Apply the concept of power factor correction to realistic circuits

Assessment – Calculate the effect(s) of connecting correction capacitors to a predominantly inductive AC circuit; e.g. pose problems in the form of the “L versus LC circuit powers” Quantitative Reasoning question.

Assessment – Determine the amount of capacitance necessary to connect to a predominantly inductive AC circuit to correct its power factor to unity; e.g. pose problems in the form of the “Correcting an arbitrary load’s power factor” and “Correcting a lagging power factor” and “Correcting a motor’s power factor” Quantitative Reasoning questions.

- **Outcome** – Independent research

Assessment – Locate electrical generator datasheets and properly interpret some of the information contained in those documents including rated output power, efficiency, and ideal power factor range.

Chapter 2


Case Tutorial

The idea behind a *Case Tutorial* is to explore new concepts by way of example. In this chapter you will read less presentation of theory compared to other Tutorial chapters, but by close observation and comparison of the given examples be able to discern patterns and principles much the same way as a scientific experimenter. Hopefully you will find these cases illuminating, and a good supplement to text-based tutorials.


These examples also serve well as challenges following your reading of the other Tutorial(s) in this module – can you explain *why* the circuits behave as they do?

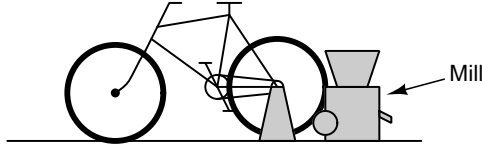2.1 Example: bicycle-driven grain mill

An engineer wants to build a machine useful to people living in rural areas of the world with no electricity service, to be able to grind their own grain using human muscle power. The invention is a bicycle-driven grain mill, where the rear wheel of the bicycle contacts a wheel on the grain mill which turns the grinding stone to convert grain into flour:



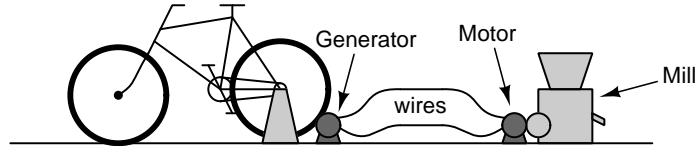
This machine works well, but then the engineer has another idea. Why not couple the bicycle to an electrical generator, then send that energy to a motor which can drive the mill at some remote location? This way the mill could be located within a food-preparation area and not have to be in the same place as the bicycle.




When tested, it is found that this system does not work as well as the first. The same effort expended on the bicycle now is only able to grind about 75% of the grain as the previous (simpler) system. The only advantage of the electric system is that the people baking bread have found they can use the heat dissipated by the electric motor and the heat dissipated by the generator to help make the dough rise in cool-weather conditions (i.e. by placing the rising dough on the housing of each electrical machine).

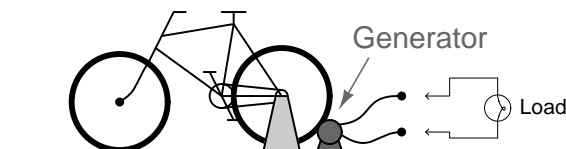2.2 Example: bicycle-driven loads


An AC generator is coupled to the rear wheel of a bicycle to allow a person to spin it using the power of their legs. The experiment will be to test the function of this generator powering different loads:



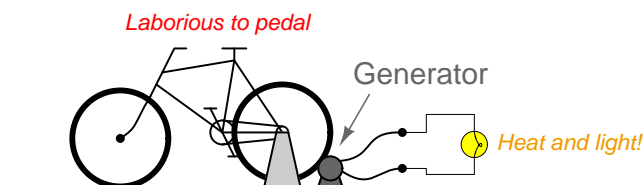
When cranked at a moderate speed, the generator outputs 120 VAC at 60 Hz. Connected to a 60 Watt incandescent lamp, an ammeter registers 0.5 Amperes of current and the lamp glows brightly, growing warm as it does. The bicyclist also notes that substantial effort is required to maintain this moderate pace.



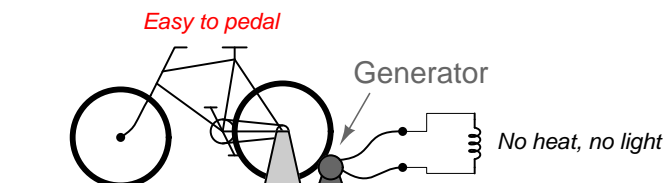Next, a 637 milli-Henry inductor is exchanged for the incandescent lamp and the experiment re-run. Once again, the ammeter registers 0.5 Amperes of current at 120 Volts (60 Hz). However, two noteworthy details are evident: the bicycle is *much* easier to pedal at the same moderate speed, and the inductor does not become warm like the lamp did.



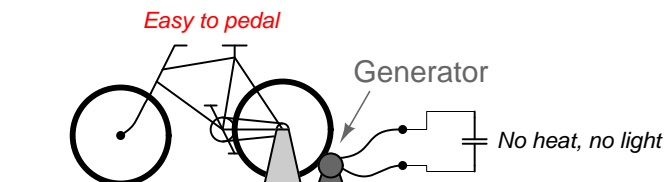Next, an 11.05 μF capacitor is exchanged for the inductor and the experiment re-run. The ammeter once again registers 0.5 Amperes at 120 Volts (60 Hz), and once again it is noted that the bicycle is very easy to pedal and there is no sensible heat dissipated at the load.



2.3 Example: electric versus gasoline car efficiency

The following examples compare energy conversion efficiencies from raw fuel to kinetic energy of a moving vehicle:

Typical gasoline-engine automobile:

Energy conversion	Efficiency
Crude oil refined into gasoline	86.5%
Typical gasoline engine	20%
Total efficiency	17.3%

Typical diesel-engine automobile:

Energy conversion	Efficiency
Crude oil refined into diesel	89.9%
Typical diesel engine	30%
Total efficiency	26.97%

Battery-electric automobile powered entirely by coal:

Energy conversion	Efficiency
Average US coal-fired power plant	37.4%
Electrical transmission/distribution grid	94.8%
Lithium-ion batteries	99%
Electric motor and drive electronics	81.2%
Total efficiency	28.5%

Battery-electric automobile powered entirely by natural gas:

Energy conversion	Efficiency
Average combined-cycle turbine power plant	57%
Electrical transmission/distribution grid	94.8%
Lithium-ion batteries	99%
Electric motor and drive electronics	81.2%
Total efficiency	43.4%

Reasons why power plant conversion efficiencies exceed typical internal-combustion engine efficiencies include the following:

- Connected to a nation-wide power grid allows power plants to operate closer to a true steady-state condition than an automobile engine which often must contend with rapidly-varying load conditions.
- Power plant boilers and turbines operate at higher temperatures than most internal-combustion engines, increasing the Carnot efficiency limit. Supercritical boilers are an example of a thermal power-plant technology operating at exceptionally high temperatures.
- Some power plants incorporate *combined-cycle* technology (using two different types of heat engine to convert thermal energy into mechanical energy) which is only practical for large, stationary applications.

One major factor ignored in these calculations is the ability of battery-electric vehicles to *recover braking energy*. This means when an electric vehicle decelerates, its motor (normally a load) behaves as a generator (now a source), converting the vehicle's kinetic energy back into electrical energy and then into chemical energy in the battery. Thus, "braking" an electric vehicle does not waste energy in the same way that "braking" an engine-powered vehicle does (where nearly 100% of the kinetic energy becomes dissipated as heat in the brake mechanism). In stop-and-go driving applications typical of urban commutes this advantage is enormous, and is why hybrid-electric cars obtain superior fuel mileage in city driving than on highways! All the conversion efficiencies presented in the previous tables assume braking energy is completely wasted, which is not the case in battery-electric vehicles. Thus, the effective energy efficiencies of electric vehicles are even higher than what is shown – just how *much* greater depends on how the vehicle is to be driven.

Some of the sources referenced for this comparison include the following:

<https://processbarron.com/u-s-coal-power-plant-efficiency-stack/>, updated 2 March 2017.

This web page cites conversion efficiencies for various coal-fueled power plants in the United States.

Proctor, Darrell, “Another World Record for Combined Cycle Efficiency”, Power Magazine, 30 September 2018.

This article chronicles the success of a combined-cycle natural gas turbine power plant setting a then-record conversion efficiency of 63.08%.

US Energy Information Administration (EIA) State Electricity Profiles database, <https://eia.gov/electricity/state>, accessed 7 April 2020.

This web page hosts spreadsheet documents with annual data for electric power energy values in all 50 states of the United States. Conversion efficiency was calculated by subtracting “direct-use” energy (i.e. not requiring transmission or distribution) from “total supply” to arrive at grid-transmitted energy. Estimated losses were subtracted from this figure, and that difference divided by the amount of grid-transmitted energy. These efficiency figures were averaged for every year from 1996 to 2018, for six states (California, Florida, Idaho, North Carolina, Washington, and Wyoming). Interestingly, the first four of these states were within a several hundredths of a percent of each other (median = 93.97%), with Washington being about a percent higher (94.86%), and Wyoming being a few percent higher than that (97.89%).

https://batteryuniversity.com/learn/article/comparing_the_battery_with_other_power_sources/, updated 28 March 2019.


This web page lists lithium-ion batteries as having a 99% charge efficiency.

Williamson, Sheldon; Emadi, Ali; Rajashekara, Kaushik; “Comprehensive Efficiency Modeling of Electric Traction Motor Drives for Hybrid Electric Vehicle Propulsion Applications”, IEEE Transactions on Vehicular Technology, Volume 56, Number 4, July 2007.

This research paper lists conversion efficiencies for components within a typical electric-drive automobile, assuming the use of a 45 kW induction motor.

Wikipedia served as the source for some of the other conversion efficiencies including gasoline engines, diesel engines, and combined-cycle natural gas turbines.

2.4 Example: RLC circuit power factor

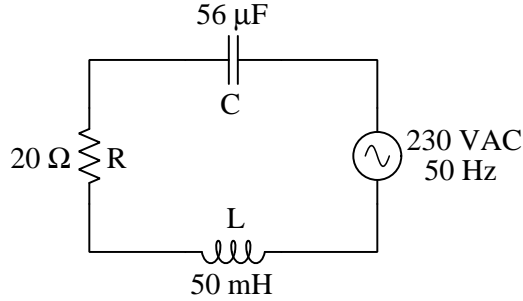

$$X_L = 2\pi(50)(50 \times 10^{-3}) = 15.7080 \Omega$$

$$Z_L = 15.7080 \Omega \angle 90^\circ$$

$$X_C = \frac{1}{2\pi(50)(56 \times 10^{-6})} = 56.8411 \Omega$$

$$Z_C = 56.8411 \Omega \angle -90^\circ$$

$$Z_T = Z_R + Z_L + Z_C$$

$$Z_T = (20 \Omega \angle 0^\circ) + (15.7080 \Omega \angle 90^\circ) + (56.8411 \Omega \angle -90^\circ) = 45.7376 \Omega \angle -64.07^\circ$$

$$I = \frac{V_{source}}{Z_T} = \frac{230 \text{ V} \angle 0^\circ}{45.7376 \Omega \angle -64.07^\circ} = 5.02868 \text{ A} \angle 64.07^\circ$$

$$V_R = IZ_R = (5.02868 \text{ A} \angle 64.07^\circ)(20 \Omega \angle 0^\circ) = 100.574 \text{ V} \angle 64.07^\circ$$

$$V_L = IZ_L = (5.02868 \text{ A} \angle 64.07^\circ)(15.7080 \Omega \angle 90^\circ) = 78.9904 \text{ V} \angle 154.07^\circ$$

$$V_C = IZ_C = (5.02868 \text{ A} \angle 64.07^\circ)(56.8411 \Omega \angle -90^\circ) = 285.836 \text{ V} \angle -25.93^\circ$$

Note: all power calculations use scalar values (i.e. current and impedance values taken from polar-form magnitudes only).

Resistor powers:

$$P_R = I^2 R = (5.02868 \text{ A})^2 (20 \Omega) = 505.753 \text{ W}$$

$$Q_R = I^2 X_R = (5.02868 \text{ A})^2 (0 \Omega) = 0 \text{ VAR}$$

$$S_R = I^2 Z_R = (5.02868 \text{ A})^2 (20 \Omega) = 505.753 \text{ VA}$$

Inductor powers:

$$P_L = I^2 R_L = (5.02868 \text{ A})^2 (0 \Omega) = 0 \text{ W}$$

$$Q_L = I^2 X_L = (5.02868 \text{ A})^2 (15.7080 \Omega) = 397.217 \text{ VAR (lagging)}$$

$$S_L = I^2 Z_L = (5.02868 \text{ A})^2 (15.7080 \Omega) = 397.217 \text{ VA}$$

Capacitor powers:

$$P_C = I^2 R_C = (5.02868 \text{ A})^2 (0 \Omega) = 0 \text{ W}$$

$$Q_C = I^2 X_C = (5.02868 \text{ A})^2 (56.8411 \Omega) = 1437.38 \text{ VAR (leading)}$$

$$S_C = I^2 Z_C = (5.02868 \text{ A})^2 (56.8411 \Omega) = 1437.38 \text{ VA}$$

Total powers:

$$P_T = P_R = 505.753 \text{ W}$$


$$Q_T = Q_C - Q_L = 1437.38 \text{ VAR (leading)} - 397.217 \text{ VAR (lagging)} = 1040.16 \text{ VAR (leading)}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = 1156.60 \text{ VA}$$

2.5 Example: power factor from V,I,P measurements

A large electrical load is outfitted with a wattmeter to measure its true power. Load voltage is 7.2 kV and load current is 24 A (both RMS), while the wattmeter measures 155 kW:

- P.F. = 0.897
- $\theta = 26.23^\circ$

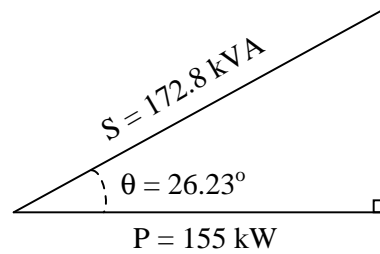

2.6 Examples: power factor correction

2.6.1 Given PF, V, I, f

An AC load exhibits a lagging power factor of 0.73 at 230 Volts and 315 Amperes, both RMS quantities. At a frequency of 60 Hz:

- Apparent power (S) = 72.45 kVA
- True power (P) = 52.89 kW
- Reactive power (Q) = 49.52 kVAR
- $\Theta = 43.11^\circ$
- Necessary parallel C size to correct power factor to unity = 2,483 μF


2.6.2 Given P, V, I, f

Another AC load (containing some inductance) consumes 15.2 MW of true power at a voltage of 115 kV and 149.8 A, both RMS quantities. At a frequency of 50 Hz:

- Apparent power (S) = 17.23 MVA
- Reactive power (Q) = 8.107 MVAR
- Power factor = 0.882 (lagging)
- $\Theta = 28.1^\circ$
- Necessary parallel C size to correct power factor to unity = 1.951 μF

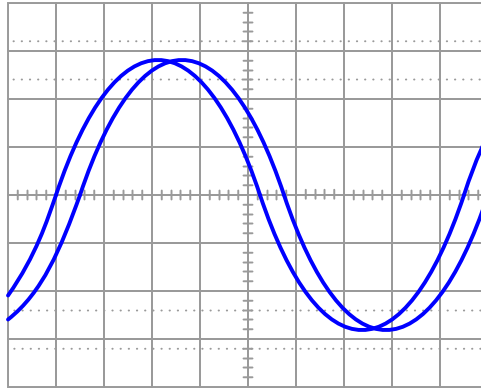2.6.3 Given oscillograph, V, I, f

A dual-trace oscilloscope is used to measure the phase shift between voltage and current for an AC load containing inductance:



Load voltage of 110 V and load current is 3.2 A (both RMS), at a frequency of 60 Hz.


- Apparent power (S) = 352 VA
- True power (P) = 328.2 W
- Reactive power (Q) = 127.2 VAR
- $\Theta = 21.2^\circ$
- Power factor = 0.932 (lagging)
- Necessary parallel C size to correct power factor to unity = 27.9 μF

Chapter 3

Simplified Tutorial

The study of electricity and of electric circuits is fundamentally an application of the more general concept of *energy transfer*. Energy may be simply defined as that which has the ability to set matter into motion, and it takes many forms. Regardless of which forms we happen to find energy in, the sum total of all energy in the universe is constant, which means energy is never created from nothing nor does it ever vanish. This foundational principle is known as the *Law of Energy Conservation*, and it has proven true at all scales from the interaction of subatomic particles to the motions of planets and stars.

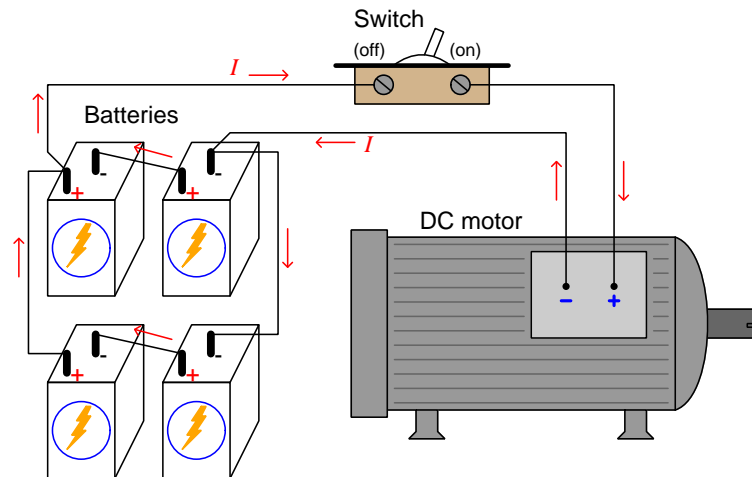To begin, let us consider a very simple circuit consisting of several electrochemical batteries powering a DC (direct current) electric motor:




As usual, “conventional-flow” current direction notation and $+/-$ voltage polarity notation helps us understand the transfer of energy in this system. We see charge carriers (electric current) entering into the $-$ terminals of the batteries and exiting from the $+$ terminals of the batteries, indicating those charge carriers enter at a low energy state and exit at a high energy state, picking up energy

from the chemicals within the batteries. We also see current entering the electric motor at its + terminal and exiting from its – terminal, indicating those charge carriers enter at high energy and exit at low energy as they deliver their energy to the motor’s shaft to do mechanical work. Electric charge carriers therefore serve as a medium for energy transfer, ultimately moving the stored energy of the batteries’ chemicals to the motor’s shaft. When the batteries are finally exhausted, current will cease and the motor’s shaft will stop turning: all the energy that used to be stored up in the batteries has now been released through the motor.

The Law of Energy Conservation is also known as the *First Law of Thermodynamics*, especially when applied to thermal systems. Another universal law of energy, just as well-founded as the Law of Energy Conservation, is the *Second Law of Thermodynamics* which simply states that energy *diffuses* (i.e. spreads out) over time. Put in other words, the Second Law declares the impossibility of transferring energy from a source to only one destination – some of that energy inevitably finds its way to other destinations too. If you imagine energy transfer being analogous to transporting water in a bucket, the First Law of Thermodynamics tells us you can never get more water out of a bucket than what you put into it, while the Second Law of Thermodynamics tells us *the bucket always leaks*.

Referring back to our electric motor circuit, we can see the Second Law in action by noting that the motor becomes hot with use. Instead of 100% of the electrical charge carriers’ energy being delivered to the motor shaft, a small portion of that energy manifests¹ as heat where it does no useful work at all. In fact, energy doesn’t just diffuse at the motor – some of it converts to heat in every part of the system! We may show this in another type of diagram, using arrows of different size to represent energy flow from one component to the other:

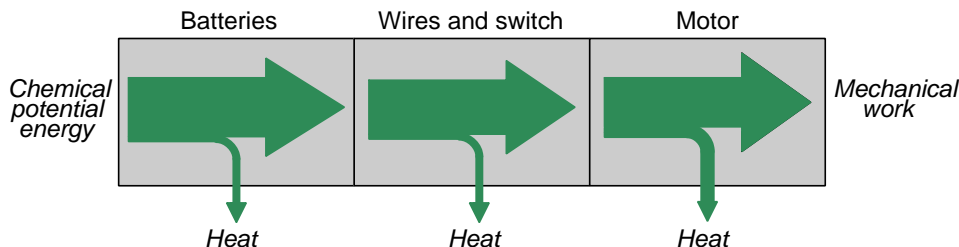


At each step in the energy transfer process, we see a small portion of the energy diverted into heat rather than to its intended purpose at the motor shaft such that the total amount of mechanical work done is guaranteed to be somewhat less than the total amount of chemical energy depleted within the batteries.

This unintentional diversion of energy into heat is called *inefficiency* or *waste*. Mathematically stated, the *efficiency* of any system is the ratio between the amount of energy converted by that system into the intended form versus the amount of energy delivered to that system:

$$\text{Efficiency} = \frac{\text{Energy converted to intended form}}{\text{Energy input to system}}$$

¹The dominant mechanism for this heat is I^2R losses in the electrical conductors: Joules Law of energy conversion from electrical to thermal as a result of electric charge carriers randomly colliding as they pass through imperfect conductors.

The Second Law of Thermodynamics applies to all physical systems and therefore over all types of electrical circuits, direct current (DC) and alternating current (AC) alike. However, AC circuits face an additional energy-conversion challenge known as *reactance*. Devices such as electric motors which convert electrical energy into useful work may be electrically modeled as resistors, in that they function as *loads* to extract energy from passing charge carriers in order to perform that work. As with any load, the energy extracted from passing charge carriers never returns to the circuit but instead is *dissipated* away from the circuit. Capacitance and inductance within AC circuits function alternately as loads and sources, periodically extracting energy from charge carriers and then infusing that energy back into charge carriers. Simply put, resistance “spends” energy while reactance “borrows” and “returns” energy:

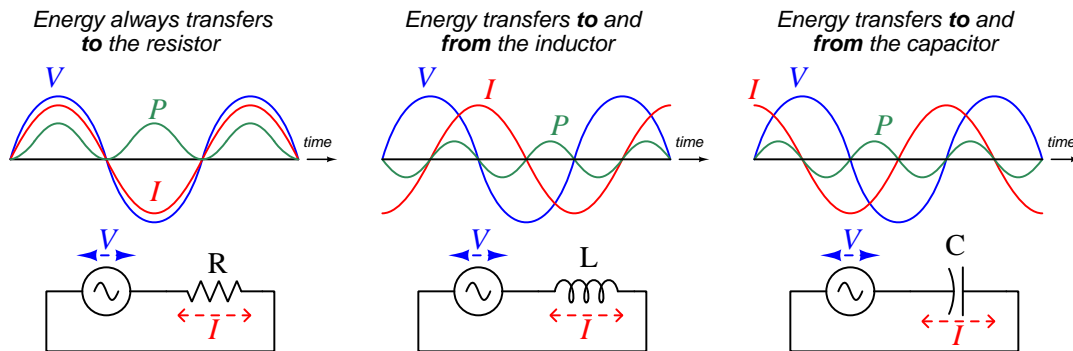

Reactance of any form in an AC circuit, be it capacitive or inductive, has the effect of making the system less effective at delivering energy because only some of it ends up being converted into useful work at the end. If the reactance happens to overshadow resistance in an AC circuit, *most* of the energy carried by charge carriers will simply alternate back and forth through the wires rather than leave the circuit to do useful work. This can be a significant problem in AC electric power systems because imperfect conductors (having some resistance) must shuttle all that energy, losing some of it as it travels in both directions (to and from the reactance).


Electric motors and other energy-conversion devices typically exhibit some amount of reactance (usually inductive), which means they do not process all the energy given but return some of it back to the circuit. In order to make sense of all this energy transfer when we calculate and measure electric power², we refer to power that is dissipated by the device as *true power* (P measured in Watts), power that is alternately stored and released as *reactive power* (Q measured in Volt-Amperes Reactive), and the combined total of true and reactive power as *apparent power* (S measured in Volt-Amperes). The mathematical ratio of true power to apparent power is called *power factor*:

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}} = \frac{P}{S}$$

True power, Apparent power, Reactive power, and Power Factor are all real (i.e. scalar) quantities rather than complex numbers, and are generally calculated from the same.

²Recall that power is simply energy per unit time. The unit of the Watt, for example, is defined as a Joule of energy transferred during every second of time.

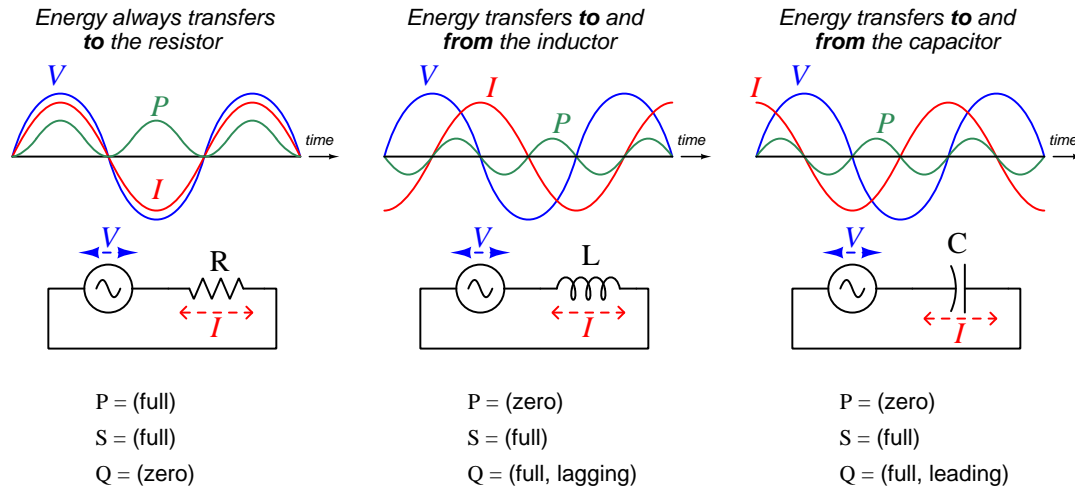
Returning to our example circuits with an ideal resistor, ideal inductor, or ideal capacitor connected to an AC source, we may compare the different types of AC power represented within each:



Only in the resistor circuit does energy leave the circuit (in the form of heat) never to return, and so we have true power (P) but no reactive power (Q). In the inductive and capacitive circuits, however, none of the energy ever leaves the circuit because it just gets sent back and forth between the reactive component and the AC source, each of those alternately acting as source and load. Therefore, with the L or C what we have is zero true power (P) but full reactive power (Q). In every case we have apparent power (S), which is the calculated value based on meter measurements of voltage and current.

When reactive power is such that the current waveform lags behind the voltage waveform, we say that the reactive power is *lagging*. Likewise for net-capacitive circuits where current leads voltage: we say that the reactive power is *leading*. Without these qualifying labels, there is no way to tell from a numerical Q value nor from a power factor ratio whether the less-than-perfect power factor results from too much inductance or from too much capacitance.

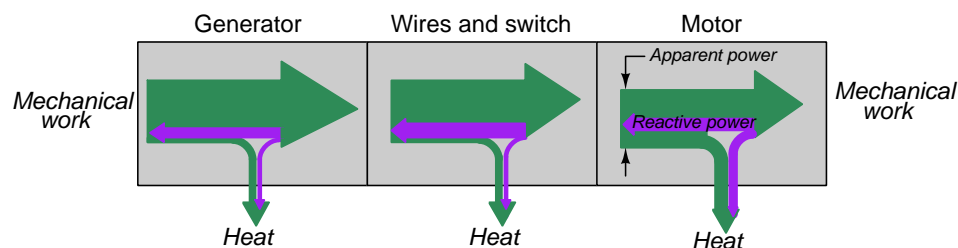Replacing batteries with an electromechanical (AC) generator and the DC motor with an AC motor, we may re-draw our energy diagram to show the relationship between true power, reactive power, apparent power, and waste in a realistic AC electric circuit:



Reactive power is not “waste” in the sense of energy leaving the system as heat, yet it is not being utilized to do the intended work. Some of that reactive power, just like some of the true (useful) power, does get converted into heat through the various inefficiencies along the way, which means more reactive power *indirectly leads to* more waste. In a large-scale electric power system this waste results in additional heating of line conductors and additional heating of generator windings.

The bucket of water analogy proves useful here: imagine someone transporting water from one reservoir to another using a bucket, dipping the bucket into one reservoir to fill it, walking over to the other reservoir with the bucket, and then emptying the bucket’s contents into that other reservoir. The bucket leaks, and this is inefficiency: water falling on the ground where we cannot use it. A poor power factor, by contrast, is the equivalent of *partially* rather than *fully* emptying the bucket at the destination reservoir, returning back to the source reservoir carrying some of the original water. The un-emptied bucket does not represent waste in the same way that water falling on the ground is wasted, but the fact that the bucket still contains water on the return trip means the bucket’s leak has more opportunity to waste water.

A perfect power factor is where no reactive power exists in the AC circuit at all, making true power equal to apparent power (i.e. power factor ratio = 1). In this scenario the AC generator and power conductors conduct only as much energy as what is truly needed at the point of use, which in turn makes the entire system more efficient. In the bucket analogy, this is when the bucket is entirely emptied at the destination and returned to the first reservoir dry: it may leak some water on the way to the destination, but at least it doesn’t also leak water on the way back.


As we see here, power factor and efficiency are *related* but not *synonymous*. To further illustrate this distinction, consider the scenario of a tree limb accidentally bridging between two power line conductors: the tree limb represents an almost perfectly resistive load with a power factor of unity (1), yet it is 0% efficient because none of the energy dissipated in the tree limb does any useful work. In the bucket analogy this is equivalent to accidentally spilling all of the bucket’s contents on the ground – there is no “reactive” water here (i.e. water carried back to the first reservoir) and therefore the power factor is at a perfect value of unity (1), but the *efficiency* is still zero. This singular example is sufficient to prove³ that power factor and efficiency cannot be the same concept.

³This is a logical technique known as *reductio ad absurdum*, where a counter-example renders an assertion absurd.

The degree to which power leaves an electric circuit (P) versus shuttles back and forth between components of that circuit (Q) depends on the phase angle separating voltage from current. When voltage and current are in-phase, as is the case with a purely resistive load, all the energy delivered by charge carriers to the resistive load becomes converted to a form where it leaves the circuit never to return. We would say such a circuit has a perfect power factor, equal to 1. Purely reactive circuits exhibit either a $+90$ or a -90 degree phase shift between voltage and current, which accounts for power alternately flowing into and away from components rather than dissipating from the circuit. We would say that a perfectly reactive circuit has a power factor of zero because none of the energy exchanged actually ever leaves the circuit. Mathematically, power factor is equal to the cosine of the angle between voltage and current waveforms, that phase angle being identical to the impedance's angle since Z is defined as the ratio of voltage to current, and polar-form complex number angles subtract when the complex numbers are divided:

$$(\text{PF}) = \cos \theta$$

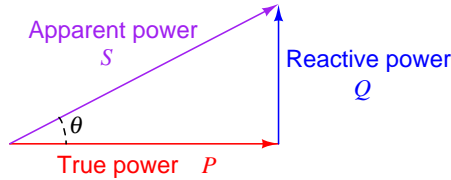We may represent power factor graphically in the form of a *phasor diagram*, where the phase shift between voltage and current in an AC circuit is represented as the angle of the vector, and the magnitude (length) of the vector represents the circuit's apparent power (S):




If we happen to know a single circuit component to be purely dissipative (e.g. a resistor), then we may conclude its power to be entirely true and non-reactive, and furthermore we may calculate that true power based on the component's resistance: $P = I^2 R$ and $P = \frac{V^2}{R}$. If we happen to know a single component to be purely reactive (e.g. a pure inductance or capacitance), then we may conclude its power to be purely reactive, and furthermore we may calculate that reactive power based on the component's reactance: $Q = I^2 X$ and $Q = \frac{V^2}{X}$. Again, these quantities are all real numbers, not complex numbers. When calculating any of these from complex voltage and current quantities, you will use the polar magnitude – otherwise known as the *absolute value* of the complex number – for V or I .

To review, apparent power (S) is the gross⁴ product of voltage and current as measured by a voltmeter and an ammeter, respectively, and is expressed in the very appropriate unit of *Volt-Amperes* (VA). True power (P) is power that actually leaves the circuit never to return, whether this is doing useful work or is merely waste, and is always expressed in *Watts* (W). Efficiency is the ratio of energy doing useful work by a system versus total energy input to that system. Reactive power (Q) is power that cycles back and forth between circuit components, never leaving the circuit, and is always expressed in *Volt-Amperes-Reactive* (VAR). Power factor is a unitless ratio of true

⁴All we mean by “gross” is that we are taking the polar magnitudes, or absolute values, of the voltage and current phasors as would be indicated by metering instruments.

power (P) to apparent power (S), and is equal to the cosine of the phase angle separating voltage and current waveforms.

Interestingly, poor power factor may be corrected by adding the complementary form of reactance to an AC circuit, preferably as close to the offending reactance as possible so that none of the power conductors need be burdened with carrying reactive power. Since most low-power-factor machines tend to be inductive (e.g. electric motors), this means added capacitance may be used to improve power factor.

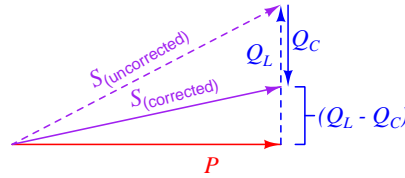

Terms commonly used to distinguish inductive Q from capacitive Q are *lagging* and *leading*, respectively, so named because of the phase relationship between current and voltage for each component type. In a typical power system where loads are connected in parallel with one or more sources and therefore all share the same voltage, it is current that distinguishes one load from another, and since current lags behind voltage for inductance we say that inductive loads have a *lagging* power factor. Capacitive loads exhibit current waveforms leading ahead of voltage, and so we say theirs is a *leading* power factor.

If inductive and capacitive reactive power are equal to each other in an AC circuit (i.e. $Q_L = Q_C$) their reactive effects will completely cancel and the power factor will be perfect, with true power equal to apparent power ($P = S$) and reactive power being zero ($Q = 0$). In an AC circuit with perfect power factor, there will be no phase shift between total voltage and total current because any amount of lagging power is perfectly canceled by an equal amount of leading power.


Determining the proper amount of capacitance to add to an inductive circuit to correct that circuit's power factor is relatively simple. First, we need to calculate the amount of reactive power exhibited by the inductance in that circuit (Q_L). If component values are known, we may do this by $Q_L = I^2 X_L$ or $Q_L = \frac{V^2}{X_L}$, using current or voltage values as indicated by meters placed in the circuit. If component values are not known, we may measure apparent power (S) and phase shift between source voltage and source current (θ), then calculate reactive power using $Q_L = S \sin \theta$. Either way, once we know the inductance's reactive power, all we need to do is add enough capacitance to the circuit so that the capacitance will have its own reactive power equal to and opposite in phase from the inductance's reactive power ($Q_C = I^2 X_C$ or $Q_C = \frac{V^2}{X_C}$).

Chapter 4

Full Tutorial

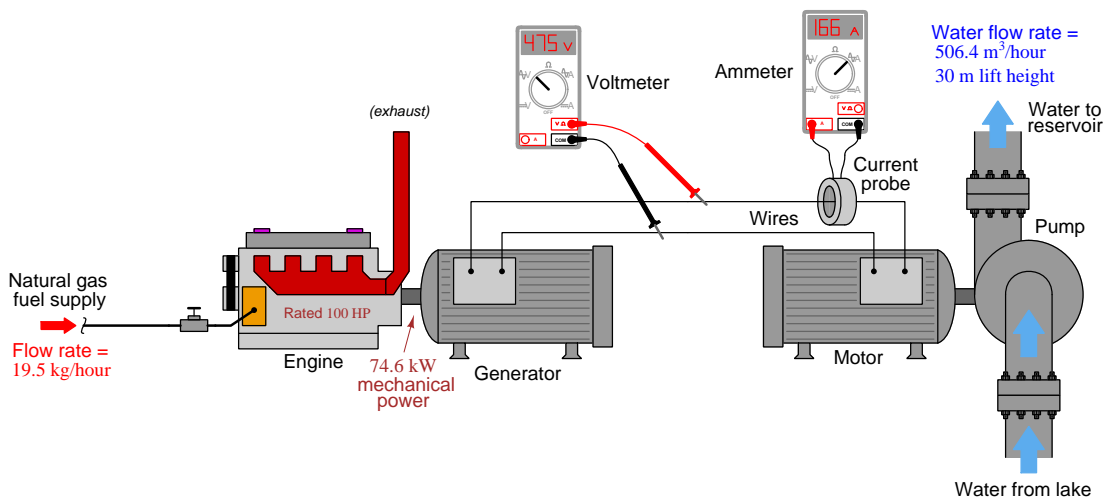4.1 Energy efficiency

Let's begin our exploration of efficiency and power factor by examining a simple AC electrical system consisting of an engine-driven AC generator, wires, and an AC electric motor connected to a water pump. The engine uses natural gas as fuel, and the pump lifts water from a lake to a reservoir atop a nearby hill.



Energy transforms from one form to another at several places in this system. At the engine the natural gas fuel is burned with air to liberate heat, representing a transformation from chemical energy to thermal energy. This heat causes air to expand, driving pistons inside the engine to produce mechanical energy at the output shaft. This mechanical energy spins the generator, which in turn translates that energy into electrical form by boosting the electrical potential of charge carriers passing through the generator's terminals. That electrical energy is delivered to the motor

where it converts again into mechanical energy to spin the pump's shaft. There, the spinning pump moves water molecules to transport them from the lake up to the water reservoir 30 meters uphill, causing the water to gain potential energy as they lift to a higher altitude.

In an ideal system all the chemical energy delivered to the engine in the form of uncombusted natural gas becomes perfectly converted into potential energy of water in the elevated reservoir. This perfect conversion of fuel energy into useful work never happens in reality, though. Although energy is conserved (i.e. none of the chemical energy in the fuel *disappears* without a trace), much of the original energy “spreads” into less-useful forms along the way. The ultimate accounting, or conservation, of energy is called the *First Law of Thermodynamics*, while the inevitable “spreading” of energy into less-useful forms is called the *Second Law of Thermodynamics*. We typically refer to the mis-directed energy as *waste*, and the forms it takes include heating of the surrounding environment, vibration, and noise.

The Second Law of Thermodynamics applies to all instances of energy conversion, and one way to gauge its action is to calculate the ratio of useful energy out versus raw energy in, that ratio being known as *efficiency*:

$$\text{Efficiency} = \frac{\text{Energy output by system in its intended form}}{\text{Energy input to system}}$$

Whatever difference exists between these two energy quantities is the energy *wasted*.

We may calculate the over-all efficiency of our water-pumping system by calculating the ratio of the water's potential energy increase as it gets pumped to the elevated reservoir to the natural gas fuel's chemical energy as it feeds the engine. A close inspection of the figures in the illustration reveal a reference to *time*, the natural gas fuel expressed as a flow rate *per hour* and the water pumping also expressed as a flow rate *per hour*. Energy per unit time is technically known as *power*, and so long as the system operates in a steady-state condition we may regard efficiency as the ratio of output power to input power:

$$\text{Efficiency} = \frac{\text{Steady-state power out}}{\text{Steady-state power in}}$$

Output power for this system may be calculated in terms of the water's weight lifted 30 meters vertically from the lake to the reservoir. Gravitational potential energy is equal to weight times height ($E_p = Wh$), and with each cubic meter of water weighing 9800 Newtons and being lifted 30 meters from lake to reservoir, each cubic meter pumped requires 294,000 Newton-meters, or 294,000 Joules of potential energy. Pumping 506.4 cubic meters of water per hour represents a water-lifting power value of 148.88 million Joules per hour, or 41.356 kiloJoules per second. Since one Joule of work done in one second's time is equivalent to a Watt of power, this is 41.356 kiloWatts of power.

Already we can see a discrepancy in the figures, as the 100 “horsepower” engine outputs a substantially larger figure of 74.6 kiloWatts mechanical power to the generator. The difference between the engine's output power of 74.6 kW and the water's pumped power of 41.356 kW is 33.244 kW of energy wasted mostly in the form of heat (e.g. heating inside the generator, heating of water traveling through the pump). Calculating efficiency from the engine's output shaft to the water, we have:

$$\text{Efficiency} = \frac{\text{Steady-state power into useful work}}{\text{Steady-state power in}} = \frac{41.356 \text{ kW}}{74.6 \text{ kW}} = 55.44\%$$

However, the system's over-all efficiency is even worse than this when we factor in the engine's conversion of chemical energy into mechanical energy. Heat engines are notoriously inefficient, and this example is no exception. To calculate this efficiency we must mathematically convert the natural gas flow rate into an *energy rate*. Fortunately, this is easy to do if we know the *heat of combustion* for the specified fuel. Natural gas is mostly comprised of methane, and methane's heat of combustion is 55.67 megaJoules per kilogram. The illustration shows the natural gas flow rate into the engine as 19.5 kilograms per hour, and so we may calculate the chemical energy rate by simple multiplication: $55.67 \text{ MJ/kg} \times 19.5 \text{ kg/hour} = 1.0856 \times 10^9 \text{ Joules per hour}$, which is 301.55 kiloJoules per second, or 301.55 kiloWatts. The energy efficiency of the engine is now simple to calculate:

$$\text{Efficiency} = \frac{\text{Steady-state power out}}{\text{Steady-state power in}} = \frac{74.6 \text{ kW}}{301.55 \text{ kW}} = 24.74\%$$

Bear in mind that this 24.74% efficiency figure is strictly for the *engine alone*, not the entire water-pumping system. This figure is rather typical for an internal combustion engine of this size, the vast majority of the fuel's heat escaping the engine in the form of hot exhaust gases and hot air from the radiator. The over-all efficiency of our water-pumping *system* is, of course, even worse than the engine's 24.74%:

$$\text{Efficiency} = \frac{\text{Steady-state water-pumping power out}}{\text{Steady-state fuel power in}} = \frac{41.356 \text{ kW}}{301.55 \text{ kW}} = 13.71\%$$

This low efficiency figure means only 13.71% of the natural gas fuel's chemical energy actually gets translated into lifting water. The rest of that energy is wasted along the way at each energy-conversion step within the system. As you can see, the single most wasteful step in the system is the engine, and so this is where the greatest potential exists for improving the system's over-all energy efficiency. Modern thermal power plants (e.g. coal-fired, gas-fired, oil-fired) achieve conversion efficiencies upwards of 60%¹ by operating engines at very high temperatures and using multiple stages of machinery to extract mechanical energy from the heat.

¹At the time of this writing, a new world record was set for conversion efficiency at an electric power plant: 63.08% at the Nisha Nagoya gas-fired power plant in the Ama District of Aichi Prefecture in Japan using the General Electric model 7HA gas turbine engine in combination with boilers and steam turbines to recover waste heat from the gas turbine engine exhaust gases. This "combined cycle" (i.e. gas turbine plus steam turbine) design results in greater efficiency than any one machine alone could muster. Another possible route to improved energy utilization is to use the low-temperature waste heat rejected by the steam turbines for industrial purposes and/or space heating of local structures rather than dissipating that waste heat to the atmosphere, a strategy known in the power plant industry as *co-generation*, or *combined heat and power* (CHP).

4.2 Power factor


So far our analysis of this water-pumping system has excluded any electrical calculations, so let's apply what we know of voltage and current to this power problem. We know from our experiences with DC circuits that power is equal to the product of current and voltage ($P = IV$), and so we may try to calculate electrical power by multiplying the two meters' RMS readings together:

$$\text{Power} = \text{Current} \times \text{Voltage} = (166 \text{ Amperes})(475 \text{ Volts}) = 78.85 \text{ kW}$$

Something is clearly wrong here, because this power value of 78.5 kW exceeds the mechanical power input to the generator's shaft (74.6 kW). The Law of Energy Conservation tells us it should be impossible to get more energy out of a component than what we put in, and this means steady-state power out must always be less than steady-state power in.

Indeed there is an error in our calculation, but it is far from obvious. The error is assuming that power in an AC circuit is just like power in a DC circuit, when in fact it is not. Power is still energy transferred per unit time, and power is still the result of electric charge carriers flowing through a component (current) while losing or gaining potential energy across that component (voltage), but power in a DC circuit was simple to calculate when both of these quantities occurred simultaneously. In an AC circuit, both voltage and current *alternate*, and these cycles may or may not be in-step with one another.

Reviewing the differences between resistance, inductance, and capacitance, we will show here graphs of voltage (V), current (I), and power (P) for each type of AC component. Resistors are dissipative devices, with voltage drop proportional to current (Ohm's Law, $V = IR$) and no phase shift between voltage and current. Inductors are reactive devices, with voltage proportional to rate-of-change of current ($V = L \frac{dI}{dt}$) and voltage leading current by $+90^\circ$. Capacitors are also reactive devices, but with current proportional to rate-of-change of voltage ($I = C \frac{dV}{dt}$) which makes voltage lag current by -90° . Pay close attention to the green-colored plot in each of these three graphs showing power:

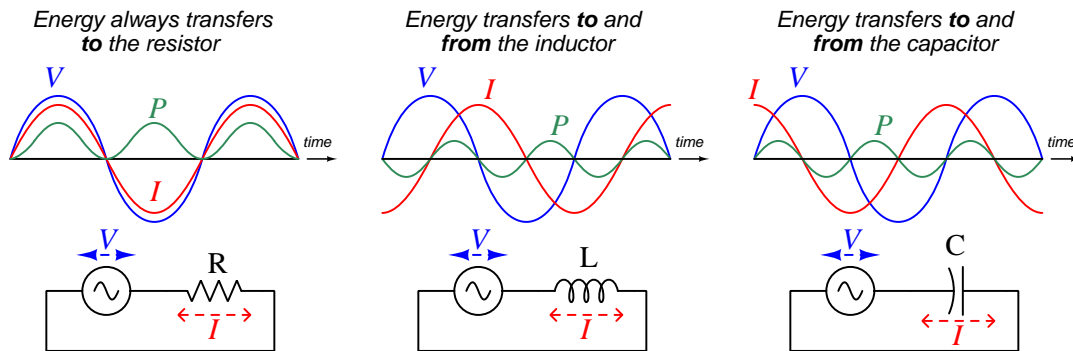


Power cycles between positive values and zero in the resistive circuit, never becoming negative. This represents pulses of energy dissipated from (i.e. leaving) the circuit. In both the inductive and capacitive circuits, however, the power waveform equally alternates between positive and negative values. This reversal of sign shows the circuit reactance alternately absorbing and returning energy

rather than dissipating energy. Note how a voltmeter and ammeter could in principle register the exact same measurements in these three circuits, but only the resistor actually transfers energy out of the circuit where it can do useful work. Therefore, calculating the product of an ammeter's and voltmeter's readings really doesn't tell us anything about how much true power that circuit passes along to a load. The product of an ammeter's and voltmeter's readings is really just an *apparent* computation of power, but not necessarily the *true* amount of power leaving the circuit.


Both the generator and the electric motor in our example system contain some inductance, owing to their construction of wire coils wrapped around iron poles. Although these machines are designed for the express purpose of converting energy between mechanical and electrical forms, the presence of inductance means some of the electrical energy doesn't actually leave the machine, but instead gets reactively shuttled back and forth with the other component(s) of the circuit. This energy, which performs no pumping of water in our system, is called *reactive power*, and it accounts for the product of our ammeter and voltmeter readings being greater than expected. Please note that reactive power is *not* a form of inefficiency because that would imply energy leaving the circuit in some non-useful form such as heat. Reactive power is simply energy shuttled back and forth between AC circuit components.

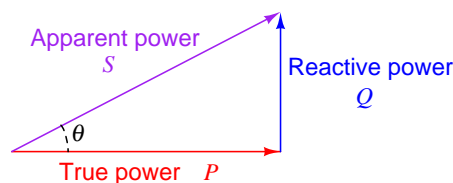The mathematical relationship between apparent power (S , expressed in *Volt-Amperes*), true power (P , expressed in *Watts*), and reactive power (Q , expressed in *Volt-Amperes Reactive*) is that of a right triangle, with angle θ representing the amount of phase shift between voltage and current:



Our previous calculation of measured current times measured voltage was actually a calculation of apparent power rather than true power, and so we should have expressed it as $S = IV = (166 \text{ A})(475 \text{ V}) = 78.85 \text{ kVA}$. The illustration of our water-pumping system lacks enough information to compute phase shift angle, and therefore we cannot tell how much true power (P) or reactive power (Q) there might be in this AC circuit.

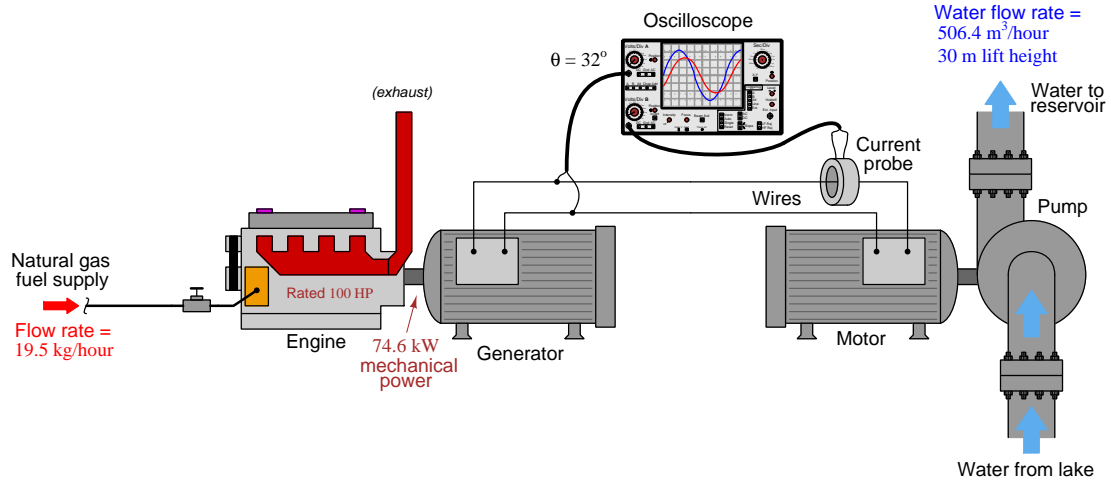We could, however, connect an oscilloscope to the circuit to measure phase shift:



From the perspective of θ in the “power triangle” we see that the cosine of θ is the ratio of true power (P) to apparent power (S) and that the sine of θ is the ratio of reactive power (Q) to apparent power (S):


$$\cos \theta = \frac{P}{S} \quad \sin \theta = \frac{Q}{S}$$

Solving for P and Q respectively in these formulae, we may take the measured 32° phase shift between voltage and current in our circuit and combine that with the computed apparent power of 78.85 kVA to calculate both true power and reactive power:

$$P = S \cos \theta = (78.85 \text{ kVA})(\cos 32^\circ) = 66.869 \text{ kW}$$

$$Q = S \sin \theta = (78.85 \text{ kVA})(\sin 32^\circ) = 41.784 \text{ kVAR}$$

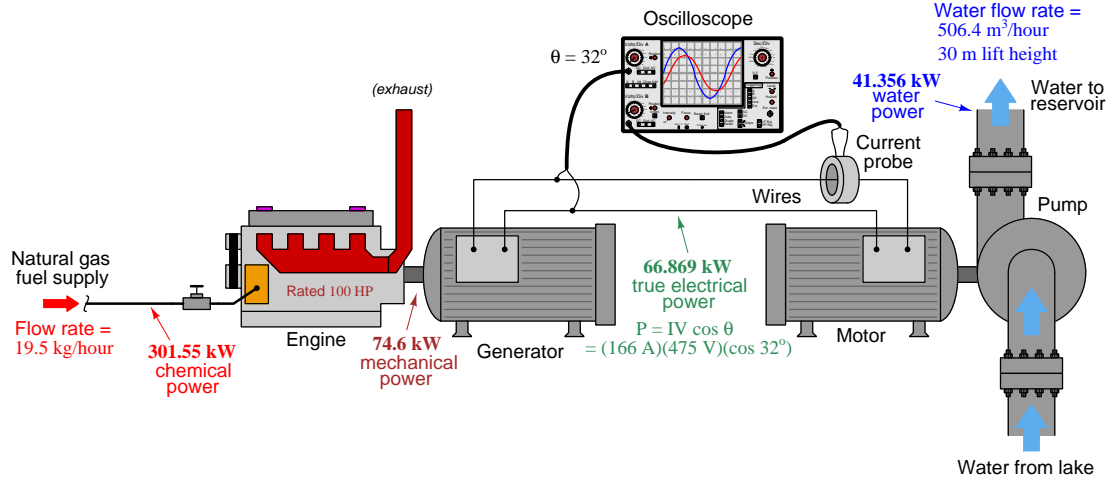Annotating the illustration with the true circuit power as well as the other power values previously calculated gives us enough information to calculate the efficiency of the engine, of the generator, and of the motor and pump combined:



$$\text{Engine efficiency} = \frac{74.6 \text{ kW}}{301.55 \text{ kW}} = 24.74\%$$


$$\text{Generator efficiency} = \frac{66.869 \text{ kW}}{74.6 \text{ kW}} = 89.63\%$$

$$\text{Motor + Pump efficiency} = \frac{41.356 \text{ kW}}{66.869 \text{ kW}} = 61.85\%$$

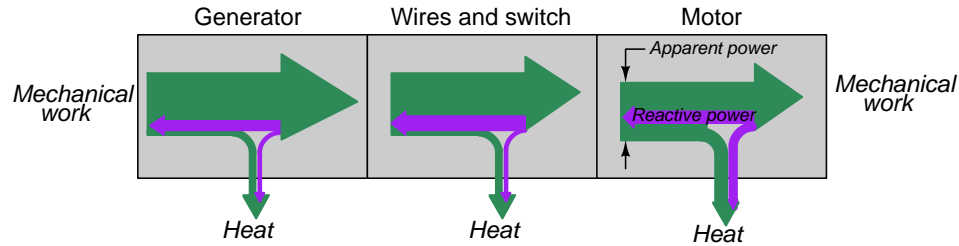4.3 How power factor affects efficiency

Although power factor and efficiency are clearly not the same concept, one of them can affect the other. The poorer the power factor is in an AC circuit, the more energy is shuttled back and forth in the circuit without leaving the circuit to do useful work. For any given amount of true power, this means a greater-than-necessary amount of apparent power. For a regulated-voltage AC circuit, as most electrical power systems are, greater apparent power means greater *current*. Therefore, as power factor approaches zero, line current increases while the system struggles to perform the same amount of useful work as before. Greater line current necessitates heavier-gauge conductors, circuit breakers and other overcurrent protection devices with higher current ratings, and other costly features. Greater line current also means more energy wasted in resistive heating of conductors ($P = I^2R$), which means more of the circuit’s true power gets wasted rather than does useful work at the load. So, *poor power factor has an indirect negative effect on efficiency*.

The following arrow diagram for a simple system where an electrical generator provides energy to a motor through connecting wires and switches illustrates this fact. Inductive reactance within the electric motor causes some of the received energy to return back to the generator, and along the way some of that returned energy gets “lost” in the form of heat:




Reactive power is not “waste” in the sense of energy leaving the system as heat, yet it is not being utilized to do the intended work. Some of that reactive power, just like some of the true (useful) power, does get converted into heat through the various inefficiencies along the way, which means more reactive power *indirectly leads to* more waste. In a large-scale electric power system this waste results in additional heating of line conductors and additional heating of generator windings.


Thankfully, there are ways to mitigate poor power factor and eliminate these additional mechanisms of “wasted” energy in AC circuits. Our review of inductive versus capacitive AC circuits shows how their respective phase shifts are completely opposite: a pure inductance exhibits a current waveform that lags -90° behind voltage, while a pure capacitance exhibits a current waveform that leads $+90^\circ$ ahead of voltage. This means the respective phase shifts of an inductance and a capacitance are exactly opposed to (i.e. 180° apart from) each other. The “leading” current drawn by a capacitor is therefore able to cancel “lagging” current drawn by an inductive load, and if just the right amount of capacitance is added in parallel with an inductive load these two reactive currents can precisely cancel each other with the result being zero reactive power, and a condition where 100% of the apparent power is true power.

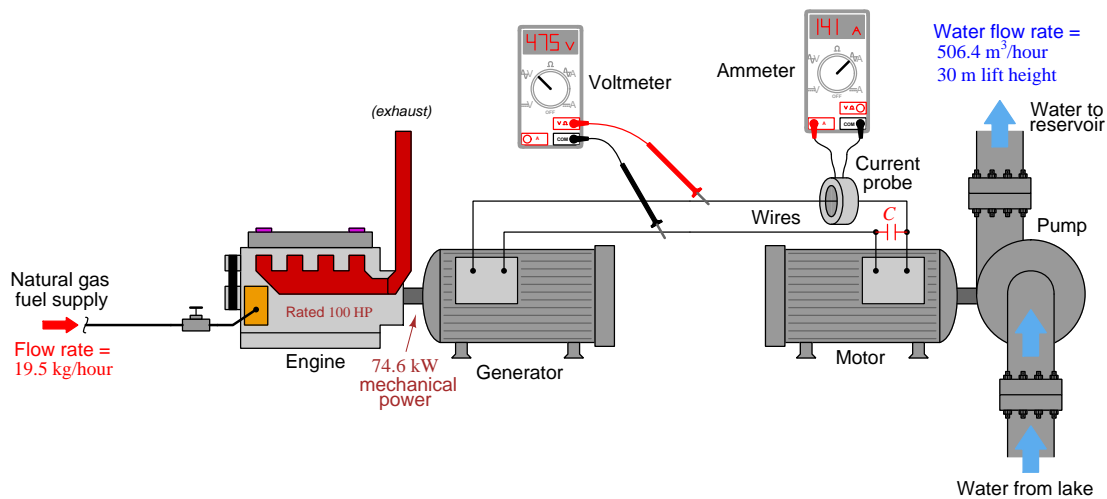4.4 Power factor correction

If we add the right amount of capacitance in parallel with the motor terminals, so as to draw enough leading current to precisely cancel the motor's lagging current, the total line current will fall to a value just large enough (140.78 Amperes) to account for the 66.869 kW of true circuit power. This will reduce (but not completely eliminate) wasteful resistive heating in the lines as well as in the generator windings. The motor's windings will still experience the full 166 Amperes of current, same as before the addition of the capacitor:



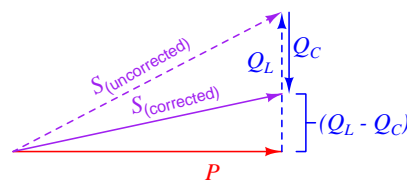The intentional addition of capacitance near an inductive load within an AC circuit is called *power factor correction*. The following phasor diagram shows the effect of adding capacitive reactance to a circuit with some inductive reactance:



In order to achieve perfect power factor correction, we must size the capacitor so that its reactive power (Q_C) is exactly equal in magnitude to the inductive load's reactive power (Q_L). Using our water-pumping system as an example, we know that the reactive power in the circuit is equal to the apparent power (S) multiplied by the sine of the 32° voltage/current phase shift:

$$Q = S \sin \theta = (78.85 \text{ kVA})(\sin 32^\circ) = 41.784 \text{ kVAR}$$

Therefore, we need to calculate the correct size of capacitor to exhibit this same amount of reactive power while energized by 475 Volts AC (RMS). Reactive power is measured in Volt-Amperes

Reactive (VAR), and so if the RMS voltage is known as it is here, the amount of reactive current (in units of Amperes Reactive) may be found simply by dividing the VAR quantity by the voltage in Volts:

$$I_C = \frac{Q_C}{V} = \frac{41.784 \text{ kVAR}}{475 \text{ V}} = 87.967 \text{ AR}$$

Ohm's Law may be applied to compute the necessary impedance of this capacitor in Ohms:

$$Z_C = \frac{V}{I} = \frac{475 \text{ V}}{87.967 \text{ A}} = 5.3998 \Omega$$

Since capacitors are assumed to be nearly 100% pure, having very little internal resistance, we may safely assume this capacitor's reactance (X) will have the same magnitude as its impedance (Z). Assuming a 60 Hz AC frequency in this system, we may solve for capacitance in Farads:

$$X_C = \frac{1}{2\pi fC}$$

$$C = \frac{1}{2\pi fX_C}$$

$$C = \frac{1}{(2\pi)(60 \text{ Hz})(5.3998 \Omega)} = 491.24 \mu\text{F}$$

In summary:

- *Efficiency* is the ratio of usable energy out versus energy in for any system or component, and it is always less than unity (1) owing to the Second Law of Thermodynamics.
- The difference between usable energy out versus energy in for any system or component is called *waste*. The sum of usable energy plus wasted energy always equals energy input to the system or component, in accordance with the Law of Energy Conservation (also known as the First Law of Thermodynamics).
- *Apparent power* (S) is the gross product of RMS voltage and RMS current as registered by independent meters. Apparent power is expressed in the unit of the Volt-Ampere (VA) as a scalar² quantity.
- *True power* (P) is the amount of power actually leaving the circuit, whether as useful work or as waste. True power is expressed in the unit of the Watt (W) as a scalar quantity.
- *Reactive power* (Q) is power that is merely exchanged back and forth between reactive components in an AC circuit, without leaving the circuit. Reactive power is expressed in the unit of the Volt-Ampere Reactive (VAR) as a scalar quantity.
- *Power factor* is the ratio of true power to apparent power in an AC circuit. It is unitless, and may range between zero and unity (0 and 1) inclusive. Power factor is mathematically equal to the cosine of the phase shift between voltage and current, this shift being equal to the phase angle of the circuit's total impedance.
- Perfect efficiency is impossible to achieve in real practice, but perfect power factor is possible.
- Poor power factor exacerbates inefficiency by giving the reactive power more opportunity to go to waste through circuit resistance and other dissipative losses.
- Poor power factor may be corrected by intentionally adding the opposite form of reactance to an AC circuit.

²By “scalar” we mean a quantity with magnitude only and no angle. In other words, we regard these as real numbers rather than complex numbers as we ordinarily would with voltage, current, and impedance in an AC circuit.

Chapter 5

Questions

This learning module, along with all others in the ModEL collection, is designed to be used in an inverted instructional environment where students independently read¹ the tutorials and attempt to answer questions on their own *prior* to the instructor's interaction with them. In place of lecture², the instructor engages with students in Socratic-style dialogue, probing and challenging their understanding of the subject matter through inquiry.

Answers are not provided for questions within this chapter, and this is by design. Solved problems may be found in the Tutorial and Derivation chapters, instead. The goal here is *independence*, and this requires students to be challenged in ways where others cannot think for them. Remember that you always have the tools of *experimentation* and *computer simulation* (e.g. SPICE) to explore concepts!

The following lists contain ideas for Socratic-style questions and challenges. Upon inspection, one will notice a strong theme of *metacognition* within these statements: they are designed to foster a regular habit of examining one's own thoughts as a means toward clearer thinking. As such these sample questions are useful both for instructor-led discussions as well as for self-study.

¹Technical reading is an essential academic skill for any technical practitioner to possess for the simple reason that the most comprehensive, accurate, and useful information to be found for developing technical competence is in textual form. Technical careers in general are characterized by the need for continuous learning to remain current with standards and technology, and therefore any technical practitioner who cannot read well is handicapped in their professional development. An excellent resource for educators on improving students' reading prowess through intentional effort and strategy is the book *Reading For Understanding – How Reading Apprenticeship Improves Disciplinary Learning in Secondary and College Classrooms* by Ruth Schoenbach, Cynthia Greenleaf, and Lynn Murphy.

²Lecture is popular as a teaching method because it is easy to implement: any reasonably articulate subject matter expert can talk to students, even with little preparation. However, it is also quite problematic. A good lecture always makes complicated concepts seem easier than they are, which is bad for students because it instills a false sense of confidence in their own understanding; reading and re-articulation requires more cognitive effort and serves to verify comprehension. A culture of teaching-by-lecture fosters a debilitating dependence upon direct personal instruction, whereas the challenges of modern life demand independent and critical thought made possible only by gathering information and perspectives from afar. Information presented in a lecture is ephemeral, easily lost to failures of memory and dictation; text is forever, and may be referenced at any time.

GENERAL CHALLENGES FOLLOWING TUTORIAL READING

- Summarize as much of the text as you can in one paragraph of your own words. A helpful strategy is to explain ideas as you would for an intelligent child: as simple as you can without compromising too much accuracy.
- Simplify a particular section of the text, for example a paragraph or even a single sentence, so as to capture the same fundamental idea in fewer words.
- Where did the text make the most sense to you? What was it about the text's presentation that made it clear?
- Identify where it might be easy for someone to misunderstand the text, and explain why you think it could be confusing.
- Identify any new concept(s) presented in the text, and explain in your own words.
- Identify any familiar concept(s) such as physical laws or principles applied or referenced in the text.
- Devise a proof of concept experiment demonstrating an important principle, physical law, or technical innovation represented in the text.
- Devise an experiment to disprove a plausible misconception.
- Did the text reveal any misconceptions you might have harbored? If so, describe the misconception(s) and the reason(s) why you now know them to be incorrect.
- Describe any useful problem-solving strategies applied in the text.
- Devise a question of your own to challenge a reader's comprehension of the text.

GENERAL FOLLOW-UP CHALLENGES FOR ASSIGNED PROBLEMS

- Identify where any fundamental laws or principles apply to the solution of this problem, especially before applying any mathematical techniques.
- Devise a thought experiment to explore the characteristics of the problem scenario, applying known laws and principles to mentally model its behavior.
- Describe in detail your own strategy for solving this problem. How did you identify and organized the given information? Did you sketch any diagrams to help frame the problem?
- Is there more than one way to solve this problem? Which method seems best to you?
- Show the work you did in solving this problem, even if the solution is incomplete or incorrect.
- What would you say was the most challenging part of this problem, and why was it so?
- Was any important information missing from the problem which you had to research or recall?
- Was there any extraneous information presented within this problem? If so, what was it and why did it not matter?
- Examine someone else's solution to identify where they applied fundamental laws or principles.
- Simplify the problem from its given form and show how to solve this simpler version of it. Examples include eliminating certain variables or conditions, altering values to simpler (usually whole) numbers, applying a limiting case (i.e. altering a variable to some extreme or ultimate value).
- For quantitative problems, identify the real-world meaning of all intermediate calculations: their units of measurement, where they fit into the scenario at hand. Annotate any diagrams or illustrations with these calculated values.
- For quantitative problems, try approaching it qualitatively instead, thinking in terms of “increase” and “decrease” rather than definite values.
- For qualitative problems, try approaching it quantitatively instead, proposing simple numerical values for the variables.
- Were there any assumptions you made while solving this problem? Would your solution change if one of those assumptions were altered?
- Identify where it would be easy for someone to go astray in attempting to solve this problem.
- Formulate your own problem based on what you learned solving this one.

GENERAL FOLLOW-UP CHALLENGES FOR EXPERIMENTS OR PROJECTS

- In what way(s) was this experiment or project easy to complete?
- Identify some of the challenges you faced in completing this experiment or project.

- Show how thorough documentation assisted in the completion of this experiment or project.
- Which fundamental laws or principles are key to this system's function?
- Identify any way(s) in which one might obtain false or otherwise misleading measurements from test equipment in this system.
- What will happen if (component X) fails (open/shorted/etc.)?
- What would have to occur to make this system unsafe?

5.1 Conceptual reasoning

These questions are designed to stimulate your analytic and synthetic thinking³. In a Socratic discussion with your instructor, the goal is for these questions to prompt an extended dialogue where assumptions are revealed, conclusions are tested, and understanding is sharpened. Your instructor may also pose additional questions based on those assigned, in order to further probe and refine your conceptual understanding.

Questions that follow are presented to challenge and probe your understanding of various concepts presented in the tutorial. These questions are intended to serve as a guide for the Socratic dialogue between yourself and the instructor. Your instructor's task is to ensure you have a sound grasp of these concepts, and the questions contained in this document are merely a means to this end. Your instructor may, at his or her discretion, alter or substitute questions for the benefit of tailoring the discussion to each student's needs. The only absolute requirement is that each student is challenged and assessed at a level equal to or greater than that represented by the documented questions.

It is far more important that you convey your *reasoning* than it is to simply convey a correct answer. For this reason, you should refrain from researching other information sources to answer questions. What matters here is that *you* are doing the thinking. If the answer is incorrect, your instructor will work with you to correct it through proper reasoning. A correct answer without an adequate explanation of how you derived that answer is unacceptable, as it does not aid the learning or assessment process.

You will note a conspicuous lack of answers given for these conceptual questions. Unlike standard textbooks where answers to every other question are given somewhere toward the back of the book, here in these learning modules students must rely on other means to check their work. The best way by far is to debate the answers with fellow students and also with the instructor during the Socratic dialogue sessions intended to be used with these learning modules. Reasoning through challenging questions with other people is an excellent tool for developing strong reasoning skills.

Another means of checking your conceptual answers, where applicable, is to use circuit simulation software to explore the effects of changes made to circuits. For example, if one of these conceptual questions challenges you to predict the effects of altering some component parameter in a circuit, you may check the validity of your work by simulating that same parameter change within software and seeing if the results agree.

³*Analytical* thinking involves the “disassembly” of an idea into its constituent parts, analogous to dissection. *Synthetic* thinking involves the “assembly” of a new idea comprised of multiple concepts, analogous to construction. Both activities are high-level cognitive skills, extremely important for effective problem-solving, necessitating frequent challenge and regular practice to fully develop.

5.1.1 Reading outline and reflections

“Reading maketh a full man; conference a ready man; and writing an exact man” – Francis Bacon

Francis Bacon’s advice is a blueprint for effective education: reading provides the learner with knowledge, writing focuses the learner’s thoughts, and critical dialogue equips the learner to confidently communicate and apply their learning. Independent acquisition and application of knowledge is a powerful skill, well worth the effort to cultivate. To this end, students should read these educational resources closely, journal their own reflections on the reading, and discuss in detail their findings with classmates and instructor(s). You should be able to do all of the following after reading any instructional text:

- ☒ Briefly SUMMARIZE THE TEXT in the form of a journal entry documenting your learning as you progress through the course of study. Share this summary in dialogue with your classmates and instructor. Journaling is an excellent self-test of thorough reading because you cannot clearly express what you have not read or did not comprehend.
- ☒ Demonstrate ACTIVE READING STRATEGIES, including verbalizing your impressions as you read, simplifying long passages to convey the same ideas using fewer words, annotating text and illustrations with your own interpretations, working through mathematical examples shown in the text, cross-referencing passages with relevant illustrations and/or other passages, identifying problem-solving strategies applied by the author, etc. Technical reading is a special case of problem-solving, and so these strategies work precisely because they help solve any problem: paying attention to your own thoughts (metacognition), eliminating unnecessary complexities, identifying what makes sense, paying close attention to details, drawing connections between separated facts, and noting the successful strategies of others.
- ☒ Identify IMPORTANT THEMES, especially GENERAL LAWS and PRINCIPLES, expounded in the text and express them in the simplest of terms as though you were teaching an intelligent child. This emphasizes connections between related topics and develops your ability to communicate complex ideas to anyone.
- ☒ Form YOUR OWN QUESTIONS based on the reading, and then pose them to your instructor and classmates for their consideration. Anticipate both correct and incorrect answers, the incorrect answer(s) assuming one or more plausible misconceptions. This helps you view the subject from different perspectives to grasp it more fully.
- ☒ Devise EXPERIMENTS to test claims presented in the reading, or to disprove misconceptions. Predict possible outcomes of these experiments, and evaluate their meanings: what result(s) would confirm, and what would constitute disproof? Running mental simulations and evaluating results is essential to scientific and diagnostic reasoning.
- ☒ Specifically identify any points you found CONFUSING. The reason for doing this is to help diagnose misconceptions and overcome barriers to learning.

5.1.2 Foundational concepts

Correct analysis and diagnosis of electric circuits begins with a proper understanding of some basic concepts. The following is a list of some important concepts referenced in this module's full tutorial. Define each of them in your own words, and be prepared to illustrate each of these concepts with a description of a practical example and/or a live demonstration.

Energy

Conservation of Energy

Second Law of Thermodynamics

Efficiency

Heat of combustion

Direct Current (DC)

Alternating Current (AC)

Resistance

Ohm's Law

Joule's Law

Inductance

Capacitance

True power

Reactive power

Apparent power

Reactance

Phase angle

Phasor diagram

□

□


□

□

□

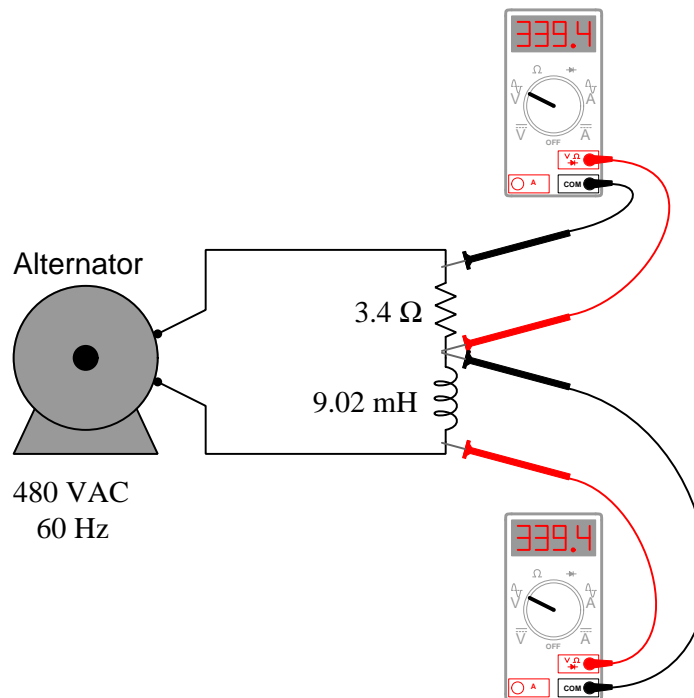5.1.3 Unequal heating

As the AC generator (alternator) powers this resistor-inductor circuit, it is found that the resistor becomes much hotter than the inductor, even though both components drop the exact same amount of voltage and carry the exact same amount of current:




Explain why there is such a remarkable difference in heat output between these two components, given their identical voltage drops and currents.

Challenges

- Suppose we had no way to sense the temperature of these components. Is there some other way to empirically demonstrate the resistor handles energy differently than the inductor?
- What will change in this circuit if the alternator's shaft is spun faster?.

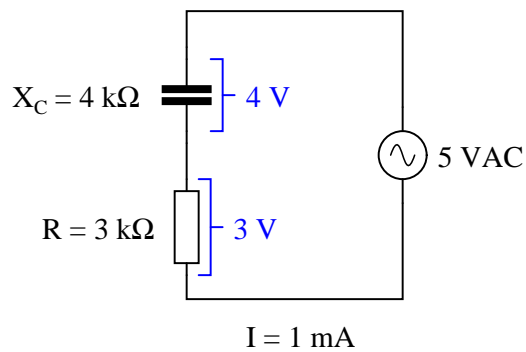5.1.4 Misconceptions about AC power

A student is pondering the behavior of a simple series RC circuit:



It is clear by now that the 4 kΩ capacitive reactance does not directly add to the 3 kΩ resistance to make 7 kΩ total. Instead, the addition of impedances is done with complex numbers (i.e. *phasors*):

$$Z_C + Z_R = Z_{total}$$

$$(4\text{k}\Omega \angle -90^\circ) + (3\text{k}\Omega \angle 0^\circ) = (5\text{k}\Omega \angle -53.13^\circ)$$


It is also clear to this student that the component voltage drops form a phasor sum as well, so that 4 Volts dropped across the capacitor in series with 3 Volts dropped across the resistor really does add up to 5 Volts total source voltage:

$$V_C + V_R = V_{total}$$

$$(4\text{V} \angle -90^\circ) + (3\text{V} \angle 0^\circ) = (5\text{V} \angle -53.13^\circ)$$

What surprises the student, though, is power. In calculating power for each component, the student arrives at 4 mW for the capacitor (4 Volts times 1 milliAmpere) and 3 mW for the resistor (3 Volts times 1 milliAmpere), but only 5 mW for the total circuit power (5 Volts times 1 milliAmpere). In DC circuits, component power dissipations *always* added, no matter how strangely their voltages and currents might be related. The student honestly expected the total power to be 7 mW, but that doesn't make sense with 5 Volts total voltage and 1 mA total current.

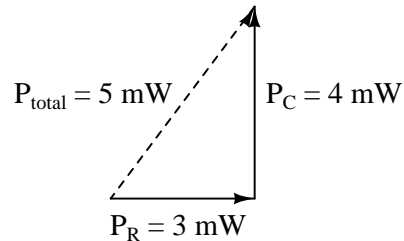Then it occurs to the student that power might add just like impedances and voltage drops. In fact, this seems to be the only way the numbers make any sense:



However, after plotting this phasor diagram the student is once again beset with doubt. According to the Law of Energy Conservation, total power in must equal total power out. If the source is inputting 5 mW of power total to this circuit, there should be no possible way that the resistor is dissipating 3 mW *and* the capacitor is dissipating 4 mW. That would constitute more energy leaving the circuit than what is entering!


What is wrong with this student's phasor diagram? How may we make sense of the figures obtained by multiplying voltage by current for each component, and for the total circuit?

Challenges

- When making the leap from DC circuit analysis to AC circuit analysis, we needed to expand on our understanding of “opposition” from just resistance (R) to include reactance (X) and (ultimately) impedance (Z). Comment on how this expansion of terms and quantities is similar when dealing with “power” in an AC circuit.

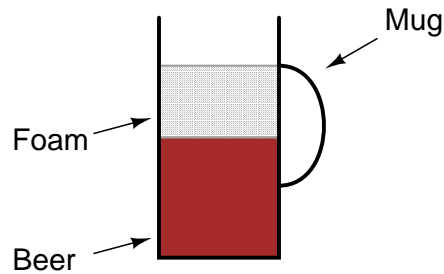5.1.5 Beer analogy for power factor

A common analogy used to describe the different types of power in AC circuits is a mug of beer that also contains foam:



Explain this analogy, relating the quantities of beer and foam to the different types of power in an AC circuit, and also why this analogy is often employed to describe the “desirability” of each power type in a circuit.

Challenges

- All analogies fail at some point. Is there a point at which the beer/foam analogy fails to properly describe the principle?

5.2 Quantitative reasoning

These questions are designed to stimulate your computational thinking. In a Socratic discussion with your instructor, the goal is for these questions to reveal your mathematical approach(es) to problem-solving so that good technique and sound reasoning may be reinforced. Your instructor may also pose additional questions based on those assigned, in order to observe your problem-solving firsthand.

Mental arithmetic and estimations are strongly encouraged for all calculations, because without these abilities you will be unable to readily detect errors caused by calculator misuse (e.g. keystroke errors).

You will note a conspicuous lack of answers given for these quantitative questions. Unlike standard textbooks where answers to every other question are given somewhere toward the back of the book, here in these learning modules students must rely on other means to check their work. My advice is to use circuit simulation software such as SPICE to check the correctness of quantitative answers. Refer to those learning modules within this collection focusing on SPICE to see worked examples which you may use directly as practice problems for your own study, and/or as templates you may modify to run your own analyses and generate your own practice problems.

Completely worked example problems found in the Tutorial may also serve as “test cases⁴” for gaining proficiency in the use of circuit simulation software, and then once that proficiency is gained you will never need to rely⁵ on an answer key!

⁴In other words, set up the circuit simulation software to analyze the same circuit examples found in the Tutorial. If the simulated results match the answers shown in the Tutorial, it confirms the simulation has properly run. If the simulated results disagree with the Tutorial’s answers, something has been set up incorrectly in the simulation software. Using every Tutorial as practice in this way will quickly develop proficiency in the use of circuit simulation software.

⁵This approach is perfectly in keeping with the instructional philosophy of these learning modules: *teaching students to be self-sufficient thinkers*. Answer keys can be useful, but it is even more useful to your long-term success to have a set of tools on hand for checking your own work, because once you have left school and are on your own, there will no longer be “answer keys” available for the problems you will have to solve.

5.2.1 Miscellaneous physical constants

Note: constants shown in **bold** type are *exact*, not approximations. Values inside of parentheses show one standard deviation (σ) of uncertainty in the final digits: for example, the magnetic permeability of free space value given as $1.25663706212(19) \times 10^{-6}$ H/m represents a center value (i.e. the location parameter) of $1.25663706212 \times 10^{-6}$ Henrys per meter with one standard deviation of uncertainty equal to $0.0000000000019 \times 10^{-6}$ Henrys per meter.

Avogadro's number (N_A) = **$6.02214076 \times 10^{23}$** per mole (mol^{-1})

Boltzmann's constant (k) = **1.380649×10^{-23}** Joules per Kelvin (J/K)

Electronic charge (e) = **$1.602176634 \times 10^{-19}$** Coulomb (C)

Faraday constant (F) = **$96,485.33212...$** $\times 10^4$ Coulombs per mole (C/mol)

Magnetic permeability of free space (μ_0) = $1.25663706212(19) \times 10^{-6}$ Henrys per meter (H/m)

Electric permittivity of free space (ϵ_0) = $8.8541878128(13) \times 10^{-12}$ Farads per meter (F/m)

Characteristic impedance of free space (Z_0) = $376.730313668(57)$ Ohms (Ω)

Gravitational constant (G) = $6.67430(15) \times 10^{-11}$ cubic meters per kilogram-seconds squared ($\text{m}^3/\text{kg}\cdot\text{s}^2$)

Molar gas constant (R) = **$8.314462618...$** Joules per mole-Kelvin (J/mol-K) = $0.08205746(14)$ liters-atmospheres per mole-Kelvin

Planck constant (h) = **$6.62607015 \times 10^{-34}$** joule-seconds (J-s)

Stefan-Boltzmann constant (σ) = **$5.670374419...$** $\times 10^{-8}$ Watts per square meter-Kelvin⁴ ($\text{W}/\text{m}^2\cdot\text{K}^4$)

Speed of light in a vacuum (c) = **$299,792,458$** meters per second (m/s) = 186282.4 miles per second (mi/s)

Note: All constants taken from NIST data "Fundamental Physical Constants – Complete Listing", from <http://physics.nist.gov/constants>, National Institute of Standards and Technology (NIST), 2018 CODATA Adjustment.

5.2.2 Introduction to spreadsheets

A powerful computational tool you are encouraged to use in your work is a *spreadsheet*. Available on most personal computers (e.g. Microsoft Excel), *spreadsheet* software performs numerical calculations based on number values and formulae entered into cells of a grid. This grid is typically arranged as lettered columns and numbered rows, with each cell of the grid identified by its column/row coordinates (e.g. cell B3, cell A8). Each cell may contain a string of text, a number value, or a mathematical formula. The spreadsheet automatically updates the results of all mathematical formulae whenever the entered number values are changed. This means it is possible to set up a spreadsheet to perform a series of calculations on entered data, and those calculations will be re-done by the computer any time the data points are edited in any way.

For example, the following spreadsheet calculates average speed based on entered values of distance traveled and time elapsed:

	A	B	C	D
1	Distance traveled	46.9	Kilometers	
2	Time elapsed	1.18	Hours	
3	Average speed	= B1 / B2	km/h	
4				
5				

Text labels contained in cells A1 through A3 and cells C1 through C3 exist solely for readability and are not involved in any calculations. Cell B1 contains a sample distance value while cell B2 contains a sample time value. The formula for computing speed is contained in cell B3. Note how this formula begins with an “equals” symbol (=), references the values for distance and speed by lettered column and numbered row coordinates (B1 and B2), and uses a forward slash symbol for division (/). The coordinates B1 and B2 function as *variables*⁶ would in an algebraic formula.

When this spreadsheet is executed, the numerical value 39.74576 will appear in cell B3 rather than the formula = B1 / B2, because 39.74576 is the computed speed value given 46.9 kilometers traveled over a period of 1.18 hours. If a different numerical value for distance is entered into cell B1 or a different value for time is entered into cell B2, cell B3’s value will automatically update. All you need to do is set up the given values and any formulae into the spreadsheet, and the computer will do all the calculations for you.

Cell B3 may be referenced by other formulae in the spreadsheet if desired, since it is a variable just like the given values contained in B1 and B2. This means it is possible to set up an entire chain of calculations, one dependent on the result of another, in order to arrive at a final value. The arrangement of the given data and formulae need not follow any pattern on the grid, which means you may place them anywhere.

⁶Spreadsheets may also provide means to attach text labels to cells for use as variable names (Microsoft Excel simply calls these labels “names”), but for simple spreadsheets such as those shown here it’s usually easier just to use the standard coordinate naming for each cell.

Common⁷ arithmetic operations available for your use in a spreadsheet include the following:

- Addition (+)
- Subtraction (-)
- Multiplication (*)
- Division (/)
- Powers (^)
- Square roots (sqrt())
- Logarithms (ln() , log10())

Parentheses may be used to ensure⁸ proper order of operations within a complex formula. Consider this example of a spreadsheet implementing the *quadratic formula*, used to solve for roots of a polynomial expression in the form of $ax^2 + bx + c$:

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

	A	B
1	x_1	= (-B4 + sqrt((B4^2) - (4*B3*B5))) / (2*B3)
2	x_2	= (-B4 - sqrt((B4^2) - (4*B3*B5))) / (2*B3)
3	a =	9
4	b =	5
5	c =	-2

This example is configured to compute roots⁹ of the polynomial $9x^2 + 5x - 2$ because the values of 9, 5, and -2 have been inserted into cells B3, B4, and B5, respectively. Once this spreadsheet has been built, though, it may be used to calculate the roots of *any* second-degree polynomial expression simply by entering the new a , b , and c coefficients into cells B3 through B5. The numerical values appearing in cells B1 and B2 will be automatically updated by the computer immediately following any changes made to the coefficients.

⁷Modern spreadsheet software offers a bewildering array of mathematical functions you may use in your computations. I recommend you consult the documentation for your particular spreadsheet for information on operations other than those listed here.

⁸Spreadsheet programs, like text-based programming languages, are designed to follow standard order of operations by default. However, my personal preference is to use parentheses even where strictly unnecessary just to make it clear to any other person viewing the formula what the intended order of operations is.

⁹Reviewing some algebra here, a *root* is a value for x that yields an overall value of zero for the polynomial. For this polynomial ($9x^2 + 5x - 2$) the two roots happen to be $x = 0.269381$ and $x = -0.82494$, with these values displayed in cells B1 and B2, respectively upon execution of the spreadsheet.

Alternatively, one could break up the long quadratic formula into smaller pieces like this:

$$y = \sqrt{b^2 - 4ac} \quad z = 2a$$

$$x = \frac{-b \pm y}{z}$$

	A	B	C
1	x_1	= (-B4 + C1) / C2	= sqrt ((B4^2) - (4*B3*B5))
2	x_2	= (-B4 - C1) / C2	= 2*B3
3	a =	9	
4	b =	5	
5	c =	-2	


Note how the square-root term (y) is calculated in cell C1, and the denominator term (z) in cell C2. This makes the two final formulae (in cells B1 and B2) simpler to interpret. The positioning of all these cells on the grid is completely arbitrary¹⁰ – all that matters is that they properly reference each other in the formulae.

Spreadsheets are particularly useful for situations where the same set of calculations representing a circuit or other system must be repeated for different initial conditions. The power of a spreadsheet is that it automates what would otherwise be a tedious set of calculations. One specific application of this is to simulate the effects of various components within a circuit failing with abnormal values (e.g. a shorted resistor simulated by making its value nearly zero; an open resistor simulated by making its value extremely large). Another application is analyzing the behavior of a circuit design given new components that are out of specification, and/or aging components experiencing drift over time.

¹⁰My personal preference is to locate all the “given” data in the upper-left cells of the spreadsheet grid (each data point flanked by a sensible name in the cell to the left and units of measurement in the cell to the right as illustrated in the first distance/time spreadsheet example), sometimes coloring them in order to clearly distinguish which cells contain entered data versus which cells contain computed results from formulae. I like to place all formulae in cells below the given data, and try to arrange them in logical order so that anyone examining my spreadsheet will be able to figure out *how* I constructed a solution. This is a general principle I believe all computer programmers should follow: *document and arrange your code to make it easy for other people to learn from it.*

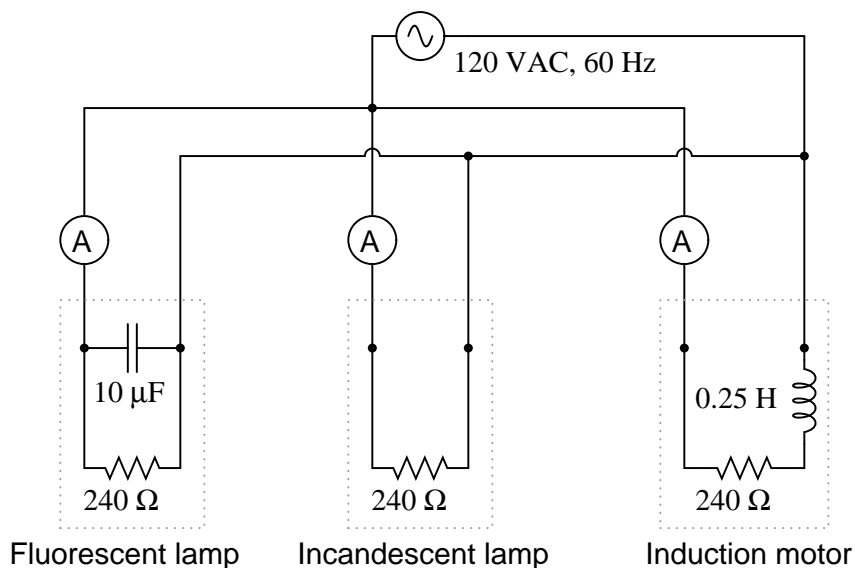5.2.3 Three AC loads

In this circuit, three common AC loads are modeled as resistances, combined with reactive components in two out of the three cases. Calculate the amount of current registered by each ammeter, and also the amount of power *dissipated* by each of the loads:



If someone were to read each of the ammeters' indications and multiply the respective currents by the figure of 120 Volts, would the resulting power figures ($P = IV$) agree with the actual power dissipations? Explain why or why not, for each load.

Challenges

- How does the “excess” current drawn by each reactive load potentially influence the size of wire needed to carry power to that load? Suppose the impedance of each load were 100 times less, resulting in 100 times as much current for each load. Would the “extra” current be significant then?

5.2.4 Power factor from wattmeter

A large single-phase electrical load is outfitted with a wattmeter to measure its true power. If the load voltage is 600 V and the load current is 48 Amperes (both RMS), calculate the load's apparent power (S). Calculate the power factor and also the phase angle between voltage and current in the circuit if the wattmeter registers 20 kW at those same voltage and current values.


Also, sketch a “power triangle” for this circuit, graphically showing the relationships between apparent power, true power, and phase angle.

Challenges

- If power factor correction were added to this circuit, which of the measured electrical values would change as a result?
- Calculate the amount of capacitance necessary to add in parallel to this load to perfectly correct its inductive (lagging) power factor. Assume a line frequency of 60 Hz.
- Suppose this load were made to be purely reactive, but draw the same amount of current from the source. Which of the measured electrical values would change as a result of this new load?
- Is it possible to determine the *efficiency* of this load from the given measurements? Explain why or why not.

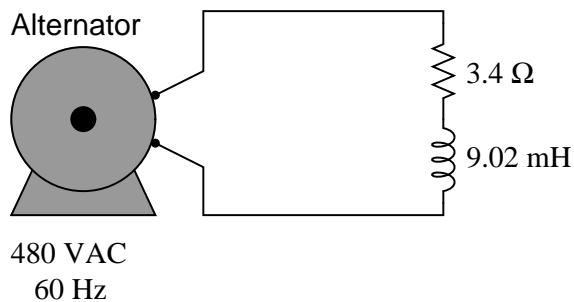5.2.5 AC generator horsepower

Calculate the amount of current in this circuit, as well as the true, reactive, and apparent power:



$$I =$$

$$P =$$

$$Q =$$

$$S =$$

Supposing the generator is 91% efficient, calculate the amount of mechanical power necessary from the “prime mover” (e.g. engine, turbine, or other machine driving the generator) to drive it, in both Watts and Horsepower:


$$P_{mech} =$$

Challenges


- Many students new to efficiency calculations either get stuck on problems such as this or obtain incorrect answers, not knowing how to reliably relate mechanical power to electrical power for generators and other electrical machinery. Explain how an *energy flow diagram* helps organize and contextualize these quantities.
- What happens to the energy delivered to the resistor from the generator?
- What happens to the energy delivered to the inductor from the generator?

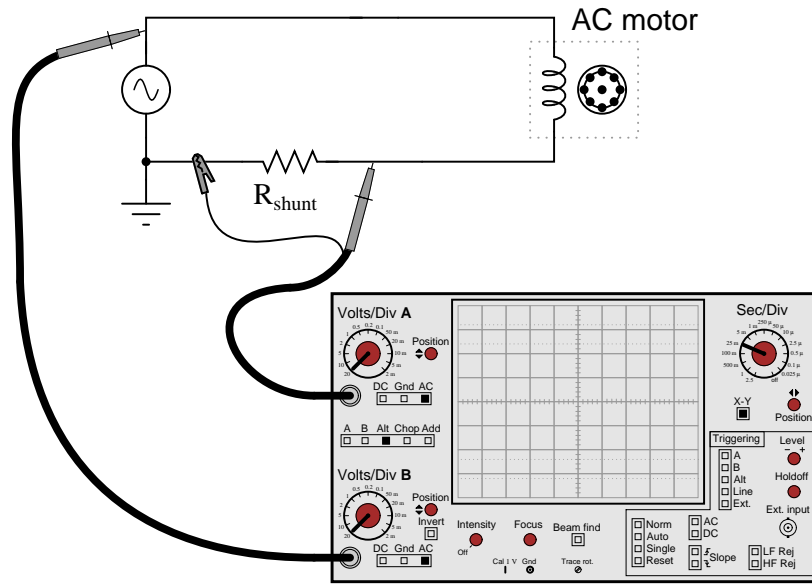5.2.6 Power factor from Lissajous figure

An oscilloscope is connected to a low-current AC motor circuit to measure both voltage and current, and plot them against one another as a Lissajous figure:



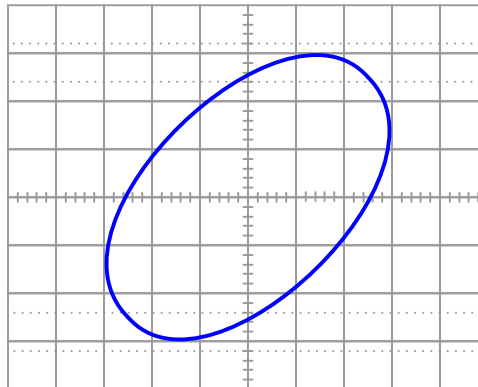The following Lissajous figure is obtained from this measurement:



From this figure, calculate the phase angle between source voltage and source current (Θ) and the power factor for this motor circuit.


Challenges

- Devise an alternative method of measuring power factor in this circuit, other than plotting a Lissajous figure.


- Explain the purpose of R_{shunt} in this circuit. Are there alternatives to using a shunt resistor to obtain the necessary measurements?
- Explain why only one of the oscilloscope's measurement channels has a ground clip connected to the power circuit.
- A common mistake when connecting oscilloscope channels to a grounded circuit is to misplace the ground clip. Identify an *incorrect* placement for the ground clip, and comment on the consequences.

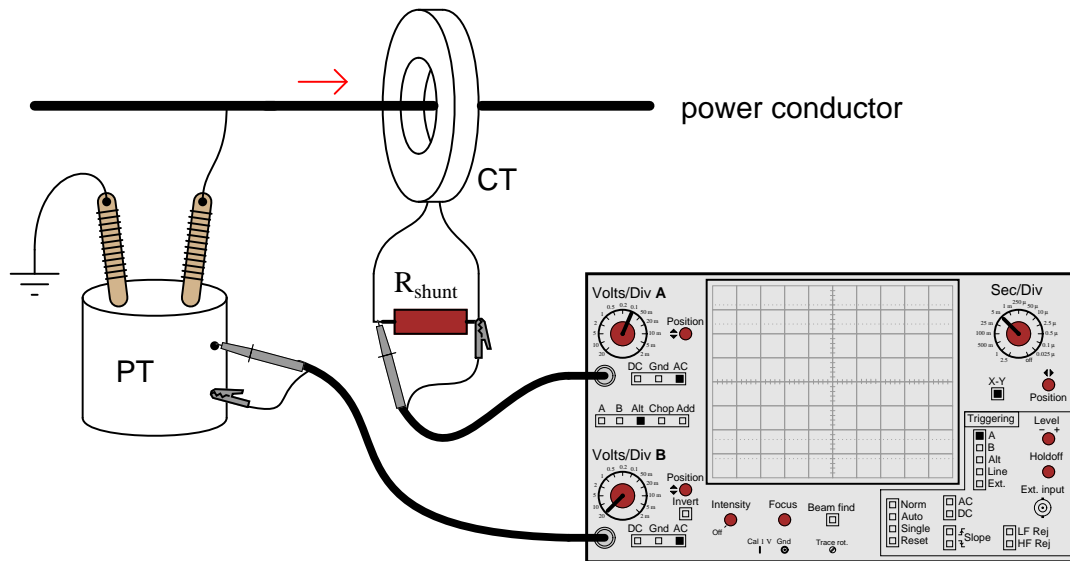5.2.7 Power factor measurement using instrument transformers

Suppose you and an electrician are tasked with measuring the power factor of a high-power AC load. The electrician is familiar with using instrument transformers (PTs and CTs) to safely measure voltage and current in high-power circuits, and you understand how to interpret the oscilloscope's image to calculate power factor.



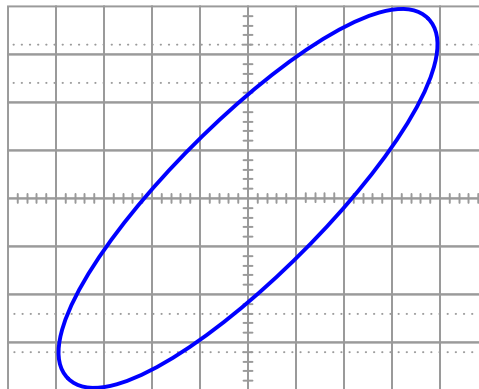After the electrician helps you safely connect to the PT and CT units, you obtain a Lissajous figure that looks like this:



Calculate the power factor of the AC load from this oscilloscope display.

Challenges

- Can we determine whether the power factor is *leading* or *lagging* from the Lissajous figure? If so, how is this done? If not, why can we not do it?

5.2.8 Hydroelectric generator ratings

A very large 3-phase alternator located at Grand Coulee Dam in Washington state has the following continuous full-power ratings:

- 600 MW power output
- 15 kV line voltage
- 23.686 kA line current


Calculate the continuous full-load apparent power for this alternator (in MVA), its continuous full-load reactive power (in MVAR), and its power factor (in percent).

Challenges

- Explain how calculations of power for three-phase systems differ from calculations of power for single-phase systems.
- The “maximum continuous overload” ratings of this same generator were 690 MW, 15 kV line voltage, and 27.239 kA line current. Does this represent the same power factor, or a different power factor?

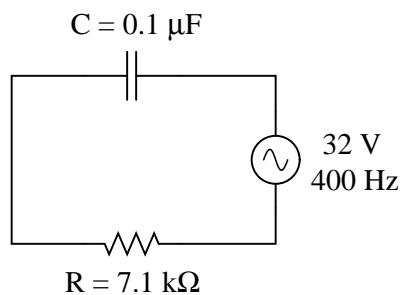5.2.9 Power factor for a capacitive circuit

Calculate the power factor of this circuit:



Challenges

- Will power factor improve or worsen as frequency increases?

5.2.10 Worsening power factor in a motor

Suppose a single-phase AC electric motor is performing mechanical work at a rate of 45 horsepower. Calculate the amount of line current necessary to power this motor if the line voltage is 460 Volts, assuming 100% motor efficiency and a power factor of 1.

Now re-calculate the necessary line current for this motor if its power factor drops to 0.65. Assume the same efficiency (100%) and the same amount of mechanical power (45 HP).

What do these calculations indicate about the importance of maintaining a high power factor value in an AC circuit?

Challenges

- What is the “extra” current in the poorer power factor scenario doing, if not contributing to the motor’s mechanical power output?
- Suppose an AC motor exhibits a good (but not perfect) power factor while operating at full load. What will happen to this motor’s power factor if it becomes mechanically unloaded?


5.2.11 L versus LC circuit powers

Calculate the apparent, true, and reactive powers for the following circuit:



- $S =$
- $P =$
- $Q =$

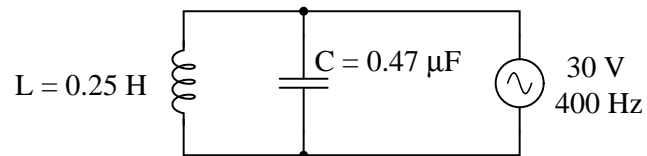Re-calculate for this circuit following the addition of a capacitor:




- $S =$
- $P =$
- $Q =$

Challenges


- Did the addition of the capacitor improve the circuit's power factor?

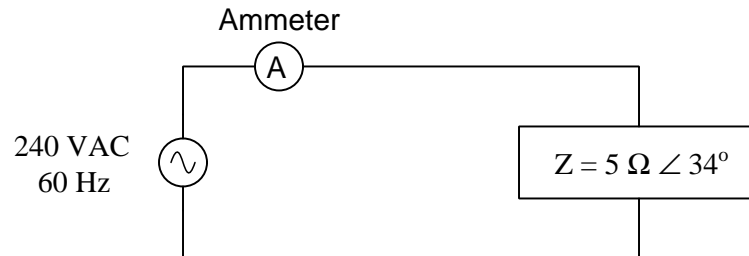5.2.12 Correcting an arbitrary load's power factor

Calculate the line current and power factor in this AC power system:



Now, calculate the line current and power factor for the same circuit after the addition of a capacitor in parallel with the load:

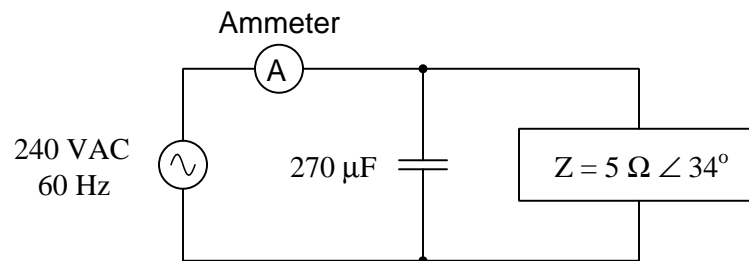**Challenges**

- Does the addition of the capacitor affect the amount of current through the 5Ω load? Why or why not?
- What would be the *ideal* capacitor value to perfectly correct power factor for this load?

5.2.13 Correcting a lagging power factor

A single-phase inductive AC load draws 13.4 Amperes of current at a voltage of 208 Volts. The phase shift between line voltage and line current is measured with an oscilloscope, and determined to be 23° . Calculate the following:

- Apparent power (S) =
- True power (P) =
- Reactive power (Q) =
- Power factor =

An electrician suggests to you that the lagging power factor may be corrected by connecting a capacitor in parallel with this load. If the capacitor is sized just right, it will exactly offset the reactive power of the inductive load, resulting in zero total reactive power and a power factor of unity (1). Calculate the size of the necessary capacitor in Farads, assuming a line frequency of 60 Hz.

Challenges

- Write an equation solving for the power factor correction capacitor size (in Farads) given any or all of the variables provided in the question (S , P , Q , f , V , P.F.).

5.2.14 Correcting a motor's power factor

A 10 horsepower single-phase electric motor operating at full rated load draws 36.15 Amperes of current at a terminal voltage of 236.0 Volts AC (60 Hz). The measured phase shift between voltage and current at the motor's terminals is 18.195° .

Calculate this motor's efficiency and its power factor.

Also, determine what you would need to add to the motor circuit to perfectly correct its power factor.


Challenges

- An all-too-common strategy employed by students when faced with problems such as this is to plug numbers into equations without regard for context and hope for the best, which never works out well. Clearly, we need a way to *organize* the information in order to make sense of what the numbers mean. Sketch a simple diagram of the motor, and annotate that diagram with the given information as well as all calculated values, to show where all the information fits.

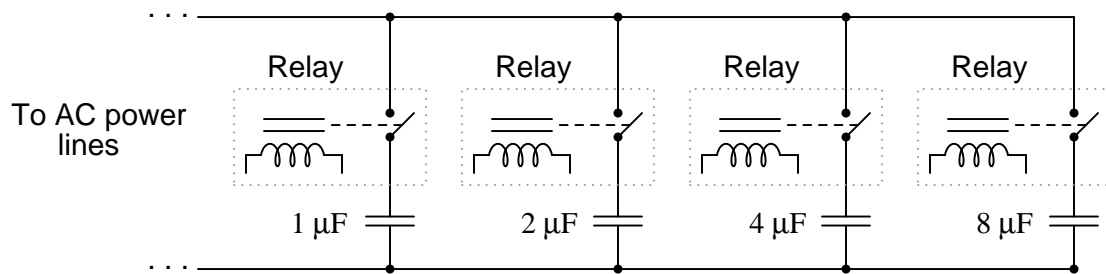5.2.15 Capacitor array

Large power distribution centers are often equipped with capacitors to correct for lagging (inductive) power factor of many industrial loads. There is never any one value for capacitance that will precisely correct for the power factor, though, because load conditions constantly change. At first it may seem that a variable capacitor would be the answer (adjustable to compensate for *any* value of lagging power factor), but variable capacitors with the ratings necessary for power line compensation would be prohibitively large and expensive.

One solution to this problem of variable capacitance uses a set of electromechanical relays with fixed-value capacitors:



Explain how a circuit such as this provides a step-variable capacitance, and determine the range of capacitance it can provide.

Assuming a line voltage of 13.8 kV RMS at a frequency of 60 Hz, calculate the range of reactive power this capacitor array is able to provide for corrective purposes.

Challenges

- What would be the effect of the $1\ \mu\text{F}$ capacitor's relay contact failing open?
- How would a human operator at the power distribution center decide which relays to open and close?

5.3 Diagnostic reasoning

These questions are designed to stimulate your deductive and inductive thinking, where you must apply general principles to specific scenarios (deductive) and also derive conclusions about the failed circuit from specific details (inductive). In a Socratic discussion with your instructor, the goal is for these questions to reinforce your recall and use of general circuit principles and also challenge your ability to integrate multiple symptoms into a sensible explanation of what's wrong in a circuit. Your instructor may also pose additional questions based on those assigned, in order to further challenge and sharpen your diagnostic abilities.

As always, your goal is to fully *explain* your analysis of each problem. Simply obtaining a correct answer is not good enough – you must also demonstrate sound reasoning in order to successfully complete the assignment. Your instructor's responsibility is to probe and challenge your understanding of the relevant principles and analytical processes in order to ensure you have a strong foundation upon which to build further understanding.

You will note a conspicuous lack of answers given for these diagnostic questions. Unlike standard textbooks where answers to every other question are given somewhere toward the back of the book, here in these learning modules students must rely on other means to check their work. The best way by far is to debate the answers with fellow students and also with the instructor during the Socratic dialogue sessions intended to be used with these learning modules. Reasoning through challenging questions with other people is an excellent tool for developing strong reasoning skills.

Another means of checking your diagnostic answers, where applicable, is to use circuit simulation software to explore the effects of faults placed in circuits. For example, if one of these diagnostic questions requires that you predict the effect of an open or a short in a circuit, you may check the validity of your work by simulating that same fault (substituting a very high resistance in place of that component for an open, and substituting a very low resistance for a short) within software and seeing if the results agree.

5.3.1 Misconceived power factor correction

Suppose an AC load is known to have an inductance of 0.5 Henrys, and an electrician wanting to improve the power factor of this circuit decides we need to install a $0.5\ \mu\text{F}$ capacitor because “*we need to balance out the lagging with an equal amount of leading*”.

Explain what is wrong with this electrician's reasoning.

Challenges

- Articulate a procedure by which one could calculate the necessary amount of capacitance to counteract the 0.5 Henrys of inductance in this load.

Appendix A

Problem-Solving Strategies

The ability to solve complex problems is arguably one of the most valuable skills one can possess, and this skill is particularly important in any science-based discipline.

- Study principles, not procedures. Don't be satisfied with merely knowing how to compute solutions – learn *why* those solutions work.
- Identify what it is you need to solve, identify all relevant data, identify all units of measurement, identify any general principles or formulae linking the given information to the solution, and then identify any “missing pieces” to a solution. Annotate all diagrams with this data.
- Sketch a diagram to help visualize the problem. When building a real system, always devise a plan for that system and analyze its function *before* constructing it.
- Follow the units of measurement and meaning of every calculation. If you are ever performing mathematical calculations as part of a problem-solving procedure, and you find yourself unable to apply each and every intermediate result to some aspect of the problem, it means you don't understand what you are doing. Properly done, every mathematical result should have practical meaning for the problem, and not just be an abstract number. You should be able to identify the proper units of measurement for each and every calculated result, and show where that result fits into the problem.
- Perform “thought experiments” to explore the effects of different conditions for theoretical problems. When troubleshooting real systems, perform *diagnostic tests* rather than visually inspecting for faults, the best diagnostic test being the one giving you the most information about the nature and/or location of the fault with the fewest steps.
- Simplify the problem until the solution becomes obvious, and then use that obvious case as a model to follow in solving the more complex version of the problem.
- Check for exceptions to see if your solution is incorrect or incomplete. A good solution will work for *all* known conditions and criteria. A good example of this is the process of testing scientific hypotheses: the task of a scientist is not to find support for a new idea, but rather to *challenge* that new idea to see if it holds up under a battery of tests. The philosophical

principle of *reductio ad absurdum* (i.e. disproving a general idea by finding a specific case where it fails) is useful here.

- Work “backward” from a hypothetical solution to a new set of given conditions.
- Add quantities to problems that are qualitative in nature, because sometimes a little math helps illuminate the scenario.
- Sketch graphs illustrating how variables relate to each other. These may be quantitative (i.e. with realistic number values) or qualitative (i.e. simply showing increases and decreases).
- Treat quantitative problems as qualitative in order to discern the relative magnitudes and/or directions of change of the relevant variables. For example, try determining what happens if a certain variable were to increase or decrease before attempting to precisely calculate quantities: how will each of the dependent variables respond, by increasing, decreasing, or remaining the same as before?
- Consider limiting cases. This works especially well for qualitative problems where you need to determine which direction a variable will change. Take the given condition and magnify that condition to an extreme degree as a way of simplifying the direction of the system’s response.
- Check your work. This means regularly testing your conclusions to see if they make sense. This does *not* mean repeating the same steps originally used to obtain the conclusion(s), but rather to use some other means to check validity. Simply repeating procedures often leads to *repeating the same errors* if any were made, which is why alternative paths are better.

Appendix B

Instructional philosophy

“The unexamined circuit is not worth energizing” – Socrates (if he had taught electricity)

These learning modules, although useful for self-study, were designed to be used in a formal learning environment where a subject-matter expert challenges students to digest the content and exercise their critical thinking abilities in the answering of questions and in the construction and testing of working circuits.

The following principles inform the instructional and assessment philosophies embodied in these learning modules:

- The first goal of education is to enhance clear and independent thought, in order that every student reach their fullest potential in a highly complex and inter-dependent world. Robust reasoning is *always* more important than particulars of any subject matter, because its application is universal.
- Literacy is fundamental to independent learning and thought because text continues to be the most efficient way to communicate complex ideas over space and time. Those who cannot read with ease are limited in their ability to acquire knowledge and perspective.
- Articulate communication is fundamental to work that is complex and interdisciplinary.
- Faulty assumptions and poor reasoning are best corrected through challenge, not presentation. The rhetorical technique of *reductio ad absurdum* (disproving an assertion by exposing an absurdity) works well to discipline student’s minds, not only to correct the problem at hand but also to learn how to detect and correct future errors.
- Important principles should be repeatedly explored and widely applied throughout a course of study, not only to reinforce their importance and help ensure their mastery, but also to showcase the interconnectedness and utility of knowledge.

These learning modules were expressly designed to be used in an “inverted” teaching environment¹ where students first read the introductory and tutorial chapters on their own, then individually attempt to answer the questions and construct working circuits according to the experiment and project guidelines. The instructor never lectures, but instead meets regularly with each individual student to review their progress, answer questions, identify misconceptions, and challenge the student to new depths of understanding through further questioning. Regular meetings between instructor and student should resemble a Socratic² dialogue, where questions serve as scalpels to dissect topics and expose assumptions. The student passes each module only after consistently demonstrating their ability to logically analyze and correctly apply all major concepts in each question or project/experiment. The instructor must be vigilant in probing each student’s understanding to ensure they are truly *reasoning* and not just *memorizing*. This is why “Challenge” points appear throughout, as prompts for students to think deeper about topics and as starting points for instructor queries. Sometimes these challenge points require additional knowledge that hasn’t been covered in the series to answer in full. This is okay, as the major purpose of the Challenges is to stimulate analysis and synthesis on the part of each student.

The instructor must possess enough mastery of the subject matter and awareness of students’ reasoning to generate their own follow-up questions to practically any student response. Even completely correct answers given by the student should be challenged by the instructor for the purpose of having students practice articulating their thoughts and defending their reasoning. Conceptual errors committed by the student should be exposed and corrected not by direct instruction, but rather by reducing the errors to an absurdity³ through well-chosen questions and thought experiments posed by the instructor. Becoming proficient at this style of instruction requires time and dedication, but the positive effects on critical thinking for both student and instructor are spectacular.

An inspection of these learning modules reveals certain unique characteristics. One of these is a bias toward thorough explanations in the tutorial chapters. Without a live instructor to explain concepts and applications to students, the text itself must fulfill this role. This philosophy results in lengthier explanations than what you might typically find in a textbook, each step of the reasoning process fully explained, including footnotes addressing common questions and concerns students raise while learning these concepts. Each tutorial seeks to not only explain each major concept in sufficient detail, but also to explain the logic of each concept and how each may be developed

¹In a traditional teaching environment, students first encounter new information via *lecture* from an expert, and then independently apply that information via *homework*. In an “inverted” course of study, students first encounter new information via *homework*, and then independently apply that information under the scrutiny of an expert. The expert’s role in lecture is to simply *explain*, but the expert’s role in an inverted session is to *challenge*, *critique*, and if necessary *explain* where gaps in understanding still exist.

²Socrates is a figure in ancient Greek philosophy famous for his unflinching style of questioning. Although he authored no texts, he appears as a character in Plato’s many writings. The essence of Socratic philosophy is to leave no question unexamined and no point of view unchallenged. While purists may argue a topic such as electric circuits is too narrow for a true Socratic-style dialogue, I would argue that the essential thought processes involved with scientific reasoning on *any* topic are not far removed from the Socratic ideal, and that students of electricity and electronics would do very well to challenge assumptions, pose thought experiments, identify fallacies, and otherwise employ the arsenal of critical thinking skills modeled by Socrates.

³This rhetorical technique is known by the Latin phrase *reductio ad absurdum*. The concept is to expose errors by counter-example, since only one solid counter-example is necessary to disprove a universal claim. As an example of this, consider the common misconception among beginning students of electricity that voltage cannot exist without current. One way to apply *reductio ad absurdum* to this statement is to ask how much current passes through a fully-charged battery connected to nothing (i.e. a clear example of voltage existing without current).

from “first principles”. Again, this reflects the goal of developing clear and independent thought in students’ minds, by showing how clear and logical thought was used to forge each concept. Students benefit from witnessing a model of clear thinking in action, and these tutorials strive to be just that.

Another characteristic of these learning modules is a lack of step-by-step instructions in the Project and Experiment chapters. Unlike many modern workbooks and laboratory guides where step-by-step instructions are prescribed for each experiment, these modules take the approach that students must learn to closely read the tutorials and apply their own reasoning to identify the appropriate experimental steps. Sometimes these steps are plainly declared in the text, just not as a set of enumerated points. At other times certain steps are implied, an example being assumed competence in test equipment use where the student should not need to be told *again* how to use their multimeter because that was thoroughly explained in previous lessons. In some circumstances no steps are given at all, leaving the entire procedure up to the student.

This lack of prescription is not a flaw, but rather a feature. Close reading and clear thinking are foundational principles of this learning series, and in keeping with this philosophy all activities are designed to *require* those behaviors. Some students may find the lack of prescription frustrating, because it demands more from them than what their previous educational experiences required. This frustration should be interpreted as an unfamiliarity with autonomous thinking, a problem which must be corrected if the student is ever to become a self-directed learner and effective problem-solver. Ultimately, the need for students to read closely and think clearly is more important both in the near-term and far-term than any specific facet of the subject matter at hand. If a student takes longer than expected to complete a module because they are forced to outline, digest, and reason on their own, so be it. The future gains enjoyed by developing this mental discipline will be well worth the additional effort and delay.

Another feature of these learning modules is that they do not treat topics in isolation. Rather, important concepts are introduced early in the series, and appear repeatedly as stepping-stones toward other concepts in subsequent modules. This helps to avoid the “compartmentalization” of knowledge, demonstrating the inter-connectedness of concepts and simultaneously reinforcing them. Each module is fairly complete in itself, reserving the beginning of its tutorial to a review of foundational concepts.

This methodology of assigning text-based modules to students for digestion and then using Socratic dialogue to assess progress and hone students’ thinking was developed over a period of several years by the author with his Electronics and Instrumentation students at the two-year college level. While decidedly unconventional and sometimes even unsettling for students accustomed to a more passive lecture environment, this instructional philosophy has proven its ability to convey conceptual mastery, foster careful analysis, and enhance employability so much better than lecture that the author refuses to ever teach by lecture again.

Problems which often go undiagnosed in a lecture environment are laid bare in this “inverted” format where students must articulate and logically defend their reasoning. This, too, may be unsettling for students accustomed to lecture sessions where the instructor cannot tell for sure who comprehends and who does not, and this vulnerability necessitates sensitivity on the part of the “inverted” session instructor in order that students never feel discouraged by having their errors exposed. *Everyone* makes mistakes from time to time, and learning is a lifelong process! Part of the instructor’s job is to build a culture of learning among the students where errors are not seen as shameful, but rather as opportunities for progress.

To this end, instructors managing courses based on these modules should adhere to the following principles:

- Student questions are always welcome and demand thorough, honest answers. The only type of question an instructor should refuse to answer is one the student should be able to easily answer on their own. Remember, *the fundamental goal of education is for each student to learn to think clearly and independently*. This requires hard work on the part of the student, which no instructor should ever circumvent. Anything done to bypass the student's responsibility to do that hard work ultimately limits that student's potential and thereby does real harm.
- It is not only permissible, but encouraged, to answer a student's question by asking questions in return, these follow-up questions designed to guide the student to reach a correct answer through their own reasoning.
- All student answers demand to be challenged by the instructor and/or by other students. This includes both correct and incorrect answers – the goal is to practice the articulation and defense of one's own reasoning.
- No reading assignment is deemed complete unless and until the student demonstrates their ability to accurately summarize the major points in their own terms. Recitation of the original text is unacceptable. This is why every module contains an "Outline and reflections" question as well as a "Foundational concepts" question in the Conceptual reasoning section, to prompt reflective reading.
- No assigned question is deemed answered unless and until the student demonstrates their ability to consistently and correctly apply the concepts to *variations* of that question. This is why module questions typically contain multiple "Challenges" suggesting different applications of the concept(s) as well as variations on the same theme(s). Instructors are encouraged to devise as many of their own "Challenges" as they are able, in order to have a multitude of ways ready to probe students' understanding.
- No assigned experiment or project is deemed complete unless and until the student demonstrates the task in action. If this cannot be done "live" before the instructor, video-recordings showing the demonstration are acceptable. All relevant safety precautions must be followed, all test equipment must be used correctly, and the student must be able to properly explain all results. The student must also successfully answer all Challenges presented by the instructor for that experiment or project.

Students learning from these modules would do well to abide by the following principles:

- No text should be considered fully and adequately read unless and until you can express every idea *in your own words, using your own examples*.
- You should always articulate your thoughts as you read the text, noting points of agreement, confusion, and epiphanies. Feel free to print the text on paper and then write your notes in the margins. Alternatively, keep a journal for your own reflections as you read. This is truly a helpful tool when digesting complicated concepts.
- Never take the easy path of highlighting or underlining important text. Instead, *summarize* and/or *comment* on the text using your own words. This actively engages your mind, allowing you to more clearly perceive points of confusion or misunderstanding on your own.
- A very helpful strategy when learning new concepts is to place yourself in the role of a teacher, if only as a mental exercise. Either explain what you have recently learned to someone else, or at least *imagine* yourself explaining what you have learned to someone else. The simple act of having to articulate new knowledge and skill forces you to take on a different perspective, and will help reveal weaknesses in your understanding.
- Perform each and every mathematical calculation and thought experiment shown in the text on your own, referring back to the text to see that your results agree. This may seem trivial and unnecessary, but it is critically important to ensuring you actually understand what is presented, especially when the concepts at hand are complicated and easy to misunderstand. Apply this same strategy to become proficient in the use of *circuit simulation software*, checking to see if your simulated results agree with the results shown in the text.
- Above all, recognize that learning is hard work, and that a certain level of frustration is unavoidable. There are times when you will struggle to grasp some of these concepts, and that struggle is a natural thing. Take heart that it will yield with persistent and varied⁴ effort, and never give up!

Students interested in using these modules for self-study will also find them beneficial, although the onus of responsibility for thoroughly reading and answering questions will of course lie with that individual alone. If a qualified instructor is not available to challenge students, a workable alternative is for students to form study groups where they challenge⁵ one another.

To high standards of education,

Tony R. Kuphaldt

⁴As the old saying goes, “Insanity is trying the same thing over and over again, expecting different results.” If you find yourself stumped by something in the text, you should attempt a different approach. Alter the thought experiment, change the mathematical parameters, do whatever you can to see the problem in a slightly different light, and then the solution will often present itself more readily.

⁵Avoid the temptation to simply share answers with study partners, as this is really counter-productive to learning. Always bear in mind that the answer to any question is far less important in the long run than the method(s) used to obtain that answer. The goal of education is to empower one’s life through the improvement of clear and independent thought, literacy, expression, and various practical skills.

Appendix C

Tools used

I am indebted to the developers of many open-source software applications in the creation of these learning modules. The following is a list of these applications with some commentary on each.

You will notice a theme common to many of these applications: a bias toward *code*. Although I am by no means an expert programmer in any computer language, I understand and appreciate the flexibility offered by code-based applications where the user (you) enters commands into a plain ASCII text file, which the software then reads and processes to create the final output. Code-based computer applications are by their very nature *extensible*, while WYSIWYG (What You See Is What You Get) applications are generally limited to whatever user interface the developer makes for you.

The GNU/Linux computer operating system

There is so much to be said about Linus Torvalds' **Linux** and Richard Stallman's **GNU** project. First, to credit just these two individuals is to fail to do justice to the *mob* of passionate volunteers who contributed to make this amazing software a reality. I first learned of **Linux** back in 1996, and have been using this operating system on my personal computers almost exclusively since then. It is *free*, it is completely *configurable*, and it permits the continued use of highly efficient **Unix** applications and scripting languages (e.g. shell scripts, Makefiles, **sed**, **awk**) developed over many decades. **Linux** not only provided me with a powerful computing platform, but its open design served to inspire my life's work of creating open-source educational resources.

Bram Moolenaar's **Vim** text editor

Writing code for any code-based computer application requires a *text editor*, which may be thought of as a word processor strictly limited to outputting plain-ASCII text files. Many good text editors exist, and one's choice of text editor seems to be a deeply personal matter within the programming world. I prefer **Vim** because it operates very similarly to **vi** which is ubiquitous on **Unix/Linux** operating systems, and because it may be entirely operated via keyboard (i.e. no mouse required) which makes it fast to use.

Donald Knuth's \TeX typesetting system

Developed in the late 1970's and early 1980's by computer scientist extraordinaire Donald Knuth to typeset his multi-volume magnum opus *The Art of Computer Programming*, this software allows the production of formatted text for screen-viewing or paper printing, all by writing plain-text code to describe how the formatted text is supposed to appear. \TeX is not just a markup language for documents, but it is also a Turing-complete programming language in and of itself, allowing useful algorithms to be created to control the production of documents. Simply put, *\TeX is a programmer's approach to word processing*. Since \TeX is controlled by code written in a plain-text file, this means anyone may read that plain-text file to see exactly how the document was created. This openness afforded by the code-based nature of \TeX makes it relatively easy to learn how other people have created their own \TeX documents. By contrast, examining a beautiful document created in a conventional WYSIWYG word processor such as Microsoft **Word** suggests nothing to the reader about *how* that document was created, or what the user might do to create something similar. As Mr. Knuth himself once quipped, conventional word processing applications should be called WYSIAYG (What You See Is *All* You Get).

Leslie Lamport's \LaTeX extensions to \TeX

Like all true programming languages, \TeX is inherently extensible. So, years after the release of \TeX to the public, Leslie Lamport decided to create a massive extension allowing easier compilation of book-length documents. The result was \LaTeX , which is the markup language used to create all ModEL module documents. You could say that \TeX is to \LaTeX as **C** is to **C++**. This means it is permissible to use any and all \TeX commands within \LaTeX source code, and it all still works. Some of the features offered by \LaTeX that would be challenging to implement in \TeX include automatic index and table-of-content creation.

Tim Edwards' **Xcircuit** drafting program

This wonderful program is what I use to create all the schematic diagrams and illustrations (but not photographic images or mathematical plots) throughout the ModEL project. It natively outputs PostScript format which is a true vector graphic format (this is why the images do not pixellate when you zoom in for a closer view), and it is so simple to use that I have never had to read the manual! Object libraries are easy to create for **Xcircuit**, being plain-text files using PostScript programming conventions. Over the years I have collected a large set of object libraries useful for drawing electrical and electronic schematics, pictorial diagrams, and other technical illustrations.

Gimp graphic image manipulation program

Essentially an open-source clone of Adobe's **PhotoShop**, I use **Gimp** to resize, crop, and convert file formats for all of the photographic images appearing in the **ModEL** modules. Although **Gimp** does offer its own scripting language (called **Script-Fu**), I have never had occasion to use it. Thus, my utilization of **Gimp** to merely crop, resize, and convert graphic images is akin to using a sword to slice bread.

SPICE circuit simulation program

SPICE is to circuit analysis as **T_EX** is to document creation: it is a form of markup language designed to describe a certain object to be processed in plain-ASCII text. When the plain-text "source file" is compiled by the software, it outputs the final result. More modern circuit analysis tools certainly exist, but I prefer **SPICE** for the following reasons: it is *free*, it is *fast*, it is *reliable*, and it is a fantastic tool for *teaching* students of electricity and electronics how to write simple code. I happen to use rather old versions of **SPICE**, version 2g6 being my "go to" application when I only require text-based output. **NGSPICE** (version 26), which is based on Berkeley **SPICE** version 3f5, is used when I require graphical output for such things as time-domain waveforms and Bode plots. In all **SPICE** example netlists I strive to use coding conventions compatible with all **SPICE** versions.

Andrew D. Hwang's ePiX mathematical visualization programming library

This amazing project is a **C++** library you may link to any **C/C++** code for the purpose of generating PostScript graphic images of mathematical functions. As a completely free and open-source project, it does all the plotting I would otherwise use a Computer Algebra System (CAS) such as **Mathematica** or **Maple** to do. It should be said that **ePiX** is *not* a Computer Algebra System like **Mathematica** or **Maple**, but merely a mathematical *visualization* tool. In other words, it won't determine integrals for you (you'll have to implement that in your own **C/C++** code!), but it can graph the results, and it does so beautifully. What I really admire about **ePiX** is that it is a **C++** programming library, which means it builds on the existing power and toolset available with that programming language. Mr. Hwang could have probably developed his own stand-alone application for mathematical plotting, but by creating a **C++** library to do the same thing he accomplished something much greater.

`gnuplot` mathematical visualization software

Another open-source tool for mathematical visualization is `gnuplot`. Interestingly, this tool is *not* part of Richard Stallman’s GNU project, its name being a coincidence. For this reason the authors prefer “gnu” *not* be capitalized at all to avoid confusion. This is a much “lighter-weight” alternative to a spreadsheet for plotting tabular data, and the fact that it easily outputs directly to an X11 console or a file in a number of different graphical formats (including PostScript) is very helpful. I typically set my `gnuplot` output format to default (X11 on my Linux PC) for quick viewing while I’m developing a visualization, then switch to PostScript file export once the visual is ready to include in the document(s) I’m writing. As with my use of `Gimp` to do rudimentary image editing, my use of `gnuplot` only scratches the surface of its capabilities, but the important points are that it’s *free* and that it *works well*.

Python programming language

Both Python and C++ find extensive use in these modules as instructional aids and exercises, but I’m listing Python here as a *tool* for myself because I use it almost daily as a *calculator*. If you open a Python interpreter console and type `from math import *` you can type mathematical expressions and have it return results just as you would on a hand calculator. Complex-number (i.e. *phasor*) arithmetic is similarly supported if you include the complex-math library (`from cmath import *`). Examples of this are shown in the Programming References chapter (if included) in each module. Of course, being a fully-featured programming language, Python also supports conditionals, loops, and other structures useful for calculation of quantities. Also, running in a console environment where all entries and returned values show as text in a chronologically-ordered list makes it easy to copy-and-paste those calculations to document exactly how they were performed.

Appendix D

Creative Commons License

Creative Commons Attribution 4.0 International Public License

By exercising the Licensed Rights (defined below), You accept and agree to be bound by the terms and conditions of this Creative Commons Attribution 4.0 International Public License (“Public License”). To the extent this Public License may be interpreted as a contract, You are granted the Licensed Rights in consideration of Your acceptance of these terms and conditions, and the Licensor grants You such rights in consideration of benefits the Licensor receives from making the Licensed Material available under these terms and conditions.

Section 1 – Definitions.

a. **Adapted Material** means material subject to Copyright and Similar Rights that is derived from or based upon the Licensed Material and in which the Licensed Material is translated, altered, arranged, transformed, or otherwise modified in a manner requiring permission under the Copyright and Similar Rights held by the Licensor. For purposes of this Public License, where the Licensed Material is a musical work, performance, or sound recording, Adapted Material is always produced where the Licensed Material is synched in timed relation with a moving image.

b. **Adapter’s License** means the license You apply to Your Copyright and Similar Rights in Your contributions to Adapted Material in accordance with the terms and conditions of this Public License.

c. **Copyright and Similar Rights** means copyright and/or similar rights closely related to copyright including, without limitation, performance, broadcast, sound recording, and Sui Generis Database Rights, without regard to how the rights are labeled or categorized. For purposes of this Public License, the rights specified in Section 2(b)(1)-(2) are not Copyright and Similar Rights.

d. **Effective Technological Measures** means those measures that, in the absence of proper authority, may not be circumvented under laws fulfilling obligations under Article 11 of the WIPO Copyright Treaty adopted on December 20, 1996, and/or similar international agreements.

e. **Exceptions and Limitations** means fair use, fair dealing, and/or any other exception or

limitation to Copyright and Similar Rights that applies to Your use of the Licensed Material.

f. **Licensed Material** means the artistic or literary work, database, or other material to which the Licensor applied this Public License.

g. **Licensed Rights** means the rights granted to You subject to the terms and conditions of this Public License, which are limited to all Copyright and Similar Rights that apply to Your use of the Licensed Material and that the Licensor has authority to license.

h. **Licensor** means the individual(s) or entity(ies) granting rights under this Public License.

i. **Share** means to provide material to the public by any means or process that requires permission under the Licensed Rights, such as reproduction, public display, public performance, distribution, dissemination, communication, or importation, and to make material available to the public including in ways that members of the public may access the material from a place and at a time individually chosen by them.

j. **Sui Generis Database Rights** means rights other than copyright resulting from Directive 96/9/EC of the European Parliament and of the Council of 11 March 1996 on the legal protection of databases, as amended and/or succeeded, as well as other essentially equivalent rights anywhere in the world.

k. **You** means the individual or entity exercising the Licensed Rights under this Public License. **Your** has a corresponding meaning.

Section 2 – Scope.

a. License grant.

1. Subject to the terms and conditions of this Public License, the Licensor hereby grants You a worldwide, royalty-free, non-sublicensable, non-exclusive, irrevocable license to exercise the Licensed Rights in the Licensed Material to:

A. reproduce and Share the Licensed Material, in whole or in part; and

B. produce, reproduce, and Share Adapted Material.

2. Exceptions and Limitations. For the avoidance of doubt, where Exceptions and Limitations apply to Your use, this Public License does not apply, and You do not need to comply with its terms and conditions.

3. Term. The term of this Public License is specified in Section 6(a).

4. Media and formats; technical modifications allowed. The Licensor authorizes You to exercise the Licensed Rights in all media and formats whether now known or hereafter created, and to make technical modifications necessary to do so. The Licensor waives and/or agrees not to assert any right or authority to forbid You from making technical modifications necessary to exercise the Licensed Rights, including technical modifications necessary to circumvent Effective Technological Measures.

For purposes of this Public License, simply making modifications authorized by this Section 2(a)(4) never produces Adapted Material.

5. Downstream recipients.

A. Offer from the Licensor – Licensed Material. Every recipient of the Licensed Material automatically receives an offer from the Licensor to exercise the Licensed Rights under the terms and conditions of this Public License.

B. No downstream restrictions. You may not offer or impose any additional or different terms or conditions on, or apply any Effective Technological Measures to, the Licensed Material if doing so restricts exercise of the Licensed Rights by any recipient of the Licensed Material.

6. No endorsement. Nothing in this Public License constitutes or may be construed as permission to assert or imply that You are, or that Your use of the Licensed Material is, connected with, or sponsored, endorsed, or granted official status by, the Licensor or others designated to receive attribution as provided in Section 3(a)(1)(A)(i).

b. Other rights.

1. Moral rights, such as the right of integrity, are not licensed under this Public License, nor are publicity, privacy, and/or other similar personality rights; however, to the extent possible, the Licensor waives and/or agrees not to assert any such rights held by the Licensor to the limited extent necessary to allow You to exercise the Licensed Rights, but not otherwise.

2. Patent and trademark rights are not licensed under this Public License.

3. To the extent possible, the Licensor waives any right to collect royalties from You for the exercise of the Licensed Rights, whether directly or through a collecting society under any voluntary or waivable statutory or compulsory licensing scheme. In all other cases the Licensor expressly reserves any right to collect such royalties.

Section 3 – License Conditions.

Your exercise of the Licensed Rights is expressly made subject to the following conditions.

a. Attribution.

1. If You Share the Licensed Material (including in modified form), You must:

A. retain the following if it is supplied by the Licensor with the Licensed Material:

i. identification of the creator(s) of the Licensed Material and any others designated to receive attribution, in any reasonable manner requested by the Licensor (including by pseudonym if designated);

ii. a copyright notice;

- iii. a notice that refers to this Public License;
- iv. a notice that refers to the disclaimer of warranties;
- v. a URI or hyperlink to the Licensed Material to the extent reasonably practicable;

B. indicate if You modified the Licensed Material and retain an indication of any previous modifications; and

C. indicate the Licensed Material is licensed under this Public License, and include the text of, or the URI or hyperlink to, this Public License.

2. You may satisfy the conditions in Section 3(a)(1) in any reasonable manner based on the medium, means, and context in which You Share the Licensed Material. For example, it may be reasonable to satisfy the conditions by providing a URI or hyperlink to a resource that includes the required information.

3. If requested by the Licensor, You must remove any of the information required by Section 3(a)(1)(A) to the extent reasonably practicable.

4. If You Share Adapted Material You produce, the Adapter's License You apply must not prevent recipients of the Adapted Material from complying with this Public License.

Section 4 – Sui Generis Database Rights.

Where the Licensed Rights include Sui Generis Database Rights that apply to Your use of the Licensed Material:

- a. for the avoidance of doubt, Section 2(a)(1) grants You the right to extract, reuse, reproduce, and Share all or a substantial portion of the contents of the database;
- b. if You include all or a substantial portion of the database contents in a database in which You have Sui Generis Database Rights, then the database in which You have Sui Generis Database Rights (but not its individual contents) is Adapted Material; and
- c. You must comply with the conditions in Section 3(a) if You Share all or a substantial portion of the contents of the database.

For the avoidance of doubt, this Section 4 supplements and does not replace Your obligations under this Public License where the Licensed Rights include other Copyright and Similar Rights.

Section 5 – Disclaimer of Warranties and Limitation of Liability.

a. Unless otherwise separately undertaken by the Licensor, to the extent possible, the Licensor offers the Licensed Material as-is and as-available, and makes no representations or warranties of any kind concerning the Licensed Material, whether express, implied, statutory, or other. This includes, without limitation, warranties of title, merchantability, fitness for a particular purpose, non-infringement, absence of latent or other defects, accuracy, or the presence or absence of errors,

whether or not known or discoverable. Where disclaimers of warranties are not allowed in full or in part, this disclaimer may not apply to You.

b. To the extent possible, in no event will the Licensor be liable to You on any legal theory (including, without limitation, negligence) or otherwise for any direct, special, indirect, incidental, consequential, punitive, exemplary, or other losses, costs, expenses, or damages arising out of this Public License or use of the Licensed Material, even if the Licensor has been advised of the possibility of such losses, costs, expenses, or damages. Where a limitation of liability is not allowed in full or in part, this limitation may not apply to You.

c. The disclaimer of warranties and limitation of liability provided above shall be interpreted in a manner that, to the extent possible, most closely approximates an absolute disclaimer and waiver of all liability.

Section 6 – Term and Termination.

a. This Public License applies for the term of the Copyright and Similar Rights licensed here. However, if You fail to comply with this Public License, then Your rights under this Public License terminate automatically.

b. Where Your right to use the Licensed Material has terminated under Section 6(a), it reinstates:

1. automatically as of the date the violation is cured, provided it is cured within 30 days of Your discovery of the violation; or
2. upon express reinstatement by the Licensor.

For the avoidance of doubt, this Section 6(b) does not affect any right the Licensor may have to seek remedies for Your violations of this Public License.

c. For the avoidance of doubt, the Licensor may also offer the Licensed Material under separate terms or conditions or stop distributing the Licensed Material at any time; however, doing so will not terminate this Public License.

d. Sections 1, 5, 6, 7, and 8 survive termination of this Public License.

Section 7 – Other Terms and Conditions.

a. The Licensor shall not be bound by any additional or different terms or conditions communicated by You unless expressly agreed.

b. Any arrangements, understandings, or agreements regarding the Licensed Material not stated herein are separate from and independent of the terms and conditions of this Public License.

Section 8 – Interpretation.

a. For the avoidance of doubt, this Public License does not, and shall not be interpreted to, reduce, limit, restrict, or impose conditions on any use of the Licensed Material that could lawfully

be made without permission under this Public License.

b. To the extent possible, if any provision of this Public License is deemed unenforceable, it shall be automatically reformed to the minimum extent necessary to make it enforceable. If the provision cannot be reformed, it shall be severed from this Public License without affecting the enforceability of the remaining terms and conditions.

c. No term or condition of this Public License will be waived and no failure to comply consented to unless expressly agreed to by the Licensor.

d. Nothing in this Public License constitutes or may be interpreted as a limitation upon, or waiver of, any privileges and immunities that apply to the Licensor or You, including from the legal processes of any jurisdiction or authority.

Creative Commons is not a party to its public licenses. Notwithstanding, Creative Commons may elect to apply one of its public licenses to material it publishes and in those instances will be considered the “Licensor.” Except for the limited purpose of indicating that material is shared under a Creative Commons public license or as otherwise permitted by the Creative Commons policies published at creativecommons.org/policies, Creative Commons does not authorize the use of the trademark “Creative Commons” or any other trademark or logo of Creative Commons without its prior written consent including, without limitation, in connection with any unauthorized modifications to any of its public licenses or any other arrangements, understandings, or agreements concerning use of licensed material. For the avoidance of doubt, this paragraph does not form part of the public licenses.

Creative Commons may be contacted at creativecommons.org.

Appendix E

References

Giancoli, Douglas C., *Physics for Scientists & Engineers*, Third Edition, Prentice Hall, Upper Saddle River, NJ, 2000.

Proctor, Darrell, “Another World Record for Combined Cycle Efficiency”, *Power* magazine, Volume 162, Number 10, pages 30-31, October 2018.

Appendix F

Version history

This is a list showing all significant additions, corrections, and other edits made to this learning module. Each entry is referenced by calendar date in reverse chronological order (newest version first), which appears on the front cover of every learning module for easy reference. Any contributors to this open-source document are listed here as well.

9-10 September 2024 – divided the Introduction chapter into sections, one with recommendations for students, one with a listing of challenging concepts, and one with recommendations for instructors. Also added a Challenge question to the “Correcting an arbitrary load’s power factor” Quantitative Reasoning question.

3 February 2024 – added a Challenge question to the “AC generator horsepower” Quantitative Reasoning question prompting students to draw an energy diagram to help solve for prime mover horsepower.

12 September 2023 – divided the Full Tutorial chapter into sections and made minor edits to its text. Also corrected an instructor note.

6-7 February 2023 – minor edits to the Simplified Tutorial, as well as numerical changes to the “Power factor from wattmeter” Quantitative Reasoning question to make it distinct from the Case Tutorial “Example: power factor from V,I,P measurements”.

28 November 2022 – placed questions at the top of the itemized list in the Introduction chapter prompting students to devise experiments related to the tutorial content.

8 May 2021 – commented out or deleted empty chapters.

11 February 2021 – minor additions to instructor notes, as well as a footnote and a minor text edits to the Simplified Tutorial. Also added Case Tutorial examples showing power factor calculations and correction calculations. Also changed order of some Quantitative Reasoning questions.

3 November 2020 – minor edit to image.0955, where I placed violet arrowheads to definitively show the direction of reactive energy that leaves the system as heat. Also, edited the Simplified

Tutorial text to make it clearer what P , Q , and S mean in real circuits.

6 October 2020 – significantly edited the Introduction chapter to make it more suitable as a pre-study guide and to provide cues useful to instructors leading “inverted” teaching sessions.

17 June 2020 – added more Foundational Concepts.

7 May 2020 – minor edit to Case Tutorial section on electric car efficiencies.

7 April 2020 – fixed improper capitalization on the word “volts” in several places. Also, added Case Tutorial examples.

6 June 2019 – added comments to both the Simplified Tutorial and the Full Tutorial about how S , Q , and P calculations may be done using real (scalar) numbers and not complex.

27 May 2019 – added more content to the Simplified Tutorial, showing how to calculate true and reactive powers for individual components, and also more detail on correcting for poor inductive power factor in an AC circuit.

26 May 2019 – added questions.

11 May 2019 – deleted an unused object from one of the illustrations – a capacitor that was suspended in space, connected to nothing.

October 2018 – completed Simplified Tutorial, clarified portions of the Introduction. Wrote a Full Tutorial.

August 2018 – added content to the Introduction.

July 2018 – document first created.

Index

- P*, 21, 31
- Q*, 21, 31
- S*, 21, 31
- Adding quantities to a qualitative problem, 70
- Annotating diagrams, 69
- Apparent power, 21, 31
- Capacitor, 30
- Checking for exceptions, 70
- Checking your work, 70
- CHP, 29
- Co-generation power plant, 29
- Code, computer, 77
- Combined heat and power, 29
- Combined-cycle power plant, 29
- Conservation of Energy, 19, 28, 30, 37
- DC, 19
- Dimensional analysis, 69
- Direct current, 19
- Dissipation, 21
- Edwards, Tim, 78
- Efficiency, 20
- Energy, 19
- First Law of Thermodynamics, 20, 28, 37
- Graph values to solve a problem, 70
- Greenleaf, Cynthia, 39
- How to teach with these modules, 72
- Hwang, Andrew D., 79
- Identify given data, 69
- Identify relevant principles, 69
- Inductor, 30
- Inefficiency, 20
- Instructions for projects and experiments, 73
- Intermediate results, 69
- Inverted instruction, 72
- Joule's Law, 20
- Knuth, Donald, 78
- Lagging, 25
- Lamport, Leslie, 78
- Leading, 25
- Limiting cases, 70
- Load, 21
- Metacognition, 44
- Moolenaar, Bram, 77
- Murphy, Lynn, 39
- Ohm's Law, 30
- Open-source, 77
- Phasor diagram, 24
- Power factor, 21
- Power factor correction, 25, 35
- Power, apparent, 21
- Power, reactive, 21
- Power, true, 21
- Problem-solving: annotate diagrams, 69
- Problem-solving: check for exceptions, 70
- Problem-solving: checking work, 70
- Problem-solving: dimensional analysis, 69
- Problem-solving: graph values, 70
- Problem-solving: identify given data, 69
- Problem-solving: identify relevant principles, 69
- Problem-solving: interpret intermediate results, 69
- Problem-solving: limiting cases, 70

- Problem-solving: qualitative to quantitative, 70
- Problem-solving: quantitative to qualitative, 70
- Problem-solving: reductio ad absurdum, 70
- Problem-solving: simplify the system, 69
- Problem-solving: thought experiment, 69
- Problem-solving: track units of measurement, 69
- Problem-solving: visually represent the system, 69
- Problem-solving: work in reverse, 70
- Qualitatively approaching a quantitative problem, 70
- Reactance, 21
- Reactive power, 21, 31
- Reading Apprenticeship, 39
- Reductio ad absurdum, 23, 70–72
- Resistor, 30
- Schoenbach, Ruth, 39
- Scientific method, 44
- Second Law of Thermodynamics, 20, 28, 37
- Simplifying a system, 69
- Socrates, 71
- Socratic dialogue, 72
- Source, 21
- SPICE, 39
- Stallman, Richard, 77
- Thermodynamics, 20, 28
- Thought experiment, 69
- Torvalds, Linus, 77
- True power, 21, 31
- Units of measurement, 69
- Visualizing a system, 69
- Volt-Ampere, 25
- Volt-Ampere (VA), 21, 31
- Volt-Ampere Reactive, 25
- Volt-Ampere Reactive (VAR), 21, 31
- Waste, 20
- Waste energy, 28
- Watt, 25
- Watt (W), 21, 31
- Work in reverse to solve a problem, 70
- WYSIWYG, 77, 78