

## Resistance, Reactance, and Impedance worksheet

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

---

This worksheet covers the following concepts:

- Phase relations of voltage and current in an inductive AC circuit. (PENDING).
- Phase relations of voltage and current in a capacitive AC circuit. (PENDING).
- Calculation of inductive reactance (PENDING).
- Calculation of capacitive reactance (PENDING).
- Combinations of reactance and resistance (PENDING).
- Vectors and trigonometry review (PENDING).


---

Resources and methods for learning about these subjects (list a few here, in preparation for your research):

---

Question 1

What will happen to the brightness of the light bulb as the iron core is moved away from the wire coil in this circuit? Explain why this happens.

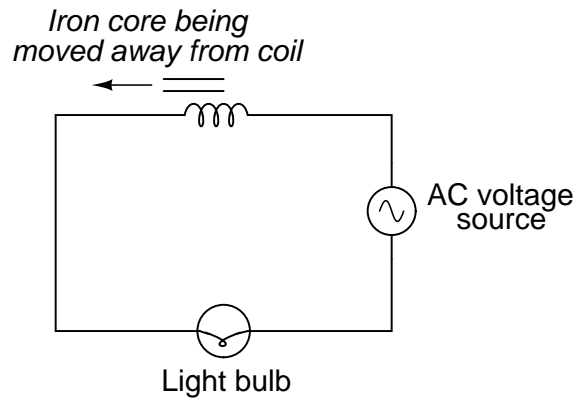

file 00095

---

Answer 1

The light bulb will glow brighter when the iron core is moved away from the wire coil, due to the change in inductive reactance ( $X_L$ ).

---

Notes 1

One direction you might want to lead your students in with this question is how AC power may be controlled using this principle. Controlling AC power with a variable *reactance* has a definite advantage over controlling AC power with a variable *resistance*: less wasted energy in the form of heat.